


Theory Assignment 4
Mengxuan Wu

1.

Function Table:

S_1	S_0	Q_3^+	Q_2^+	Q_1^+	Q_0^+	Operation
0	0	Q_3	Q_2	Q_1	Q_0	No Change
0	1	Q_3'	Q_2'	Q_1'	Q_0'	Complement the four outputs
1	0	0	0	0	0	Clear register to 0
1	1	D_3	D_2	D_1	D_0	Load parallel data

Logic Diagram:

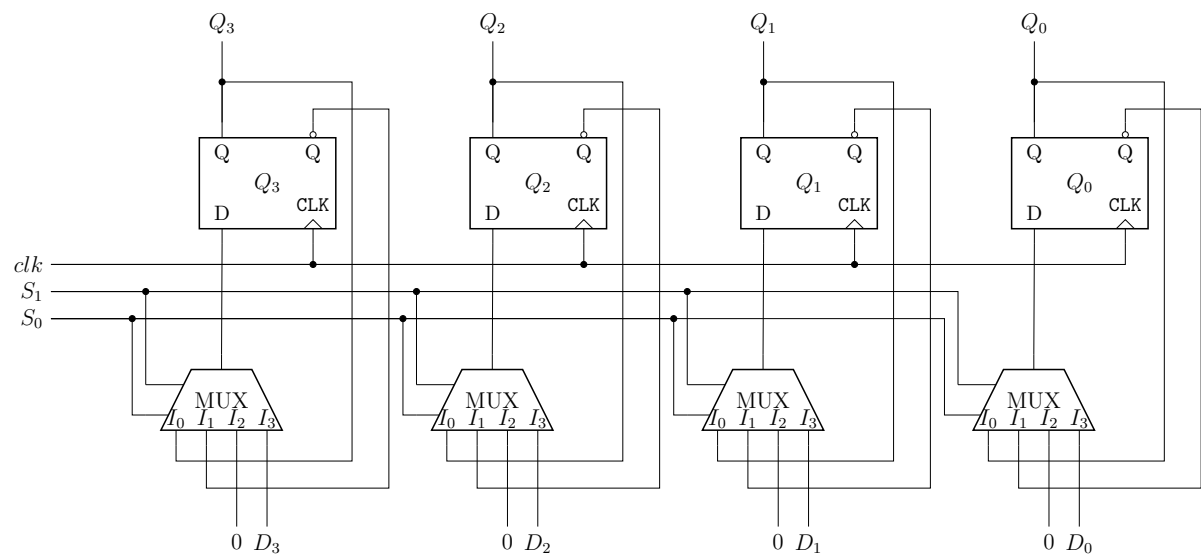

2.

With 7 possible states, we start with 3 flip-flops.

Z	Q_2	Q_1	Q_0
0	1	0	1
1	0	1	0
1	1	0	1
1	1	1	0
1	1	1	1
0	1	1	1
1	0	1	1

However, there are identical states with different outputs. We can add another flip-flop to make the circuit work.

Z	Q_3	Q_2	Q_1	Q_0
0	1	0	1	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0
0	1	1	1	1
1	0	1	1	1


Now there are no identical states with different outputs.

Karnaugh Maps:

Q_3Q_2 \ Q_1Q_0		Q_1Q_0			
		00	01	11	10
00		X	X	X	X
01		X	1	1	X
11		X	1	0	1
10		X	X	0	1

Simplified Boolean Expression:

$$Z = Q'_0 + Q'_1 + Q'_3$$

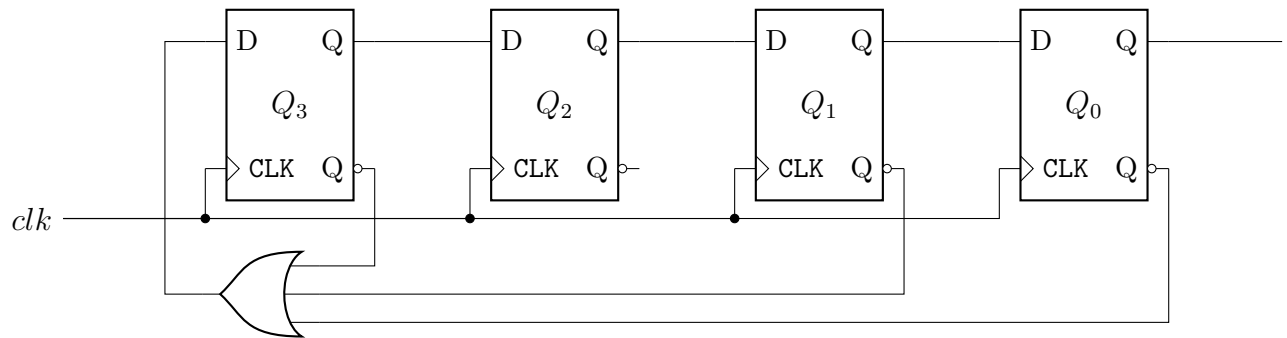Logic Diagram:**3.****State Table:**

Current State				Next State			
Q_3	Q_2	Q_1	Q_0	Q_3^+	Q_2^+	Q_1^+	Q_0^+
0	0	0	0	0	0	1	0
0	0	0	1	0	0	1	0
0	0	1	0	0	1	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	0	1	0
0	1	0	1	0	0	1	0
0	1	1	0	1	0	0	1
0	1	1	1	0	0	1	0
1	0	0	0	1	1	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	0	1	0
1	0	1	1	0	0	1	0
1	1	0	0	1	1	0	1
1	1	0	1	0	0	1	0
1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0

Karnaugh Maps:

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	0	0	0	0
01	0	0	0	1
11	1	0	0	0
10	1	1	0	0

 D_3

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	0	0	0	1
01	0	0	0	0
11	1	0	0	0
10	1	0	0	0

 D_2

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	1	1	1	1
01	1	1	1	0
11	0	1	1	1
10	0	0	1	1

 D_1

$Q_3Q_2 \backslash Q_1Q_0$	00	01	11	10
00	0	0	0	0
01	0	0	0	1
11	1	0	0	0
10	0	0	0	0


 D_0 **Simplified Boolean Expression:**

$$D_3 = Q_3Q_1'Q_0' + Q_3Q_2'Q_1' + Q_3'Q_2Q_1Q_0'$$

$$D_2 = Q_3Q_1'Q_0' + Q_3'Q_2'Q_1Q_0'$$

$$D_1 = Q_3'Q_2' + Q_3'Q_1' + Q_2Q_0 + Q_3Q_1$$

$$D_0 = Q_3Q_2Q_1'Q_0' + Q_3'Q_2Q_1Q_0'$$

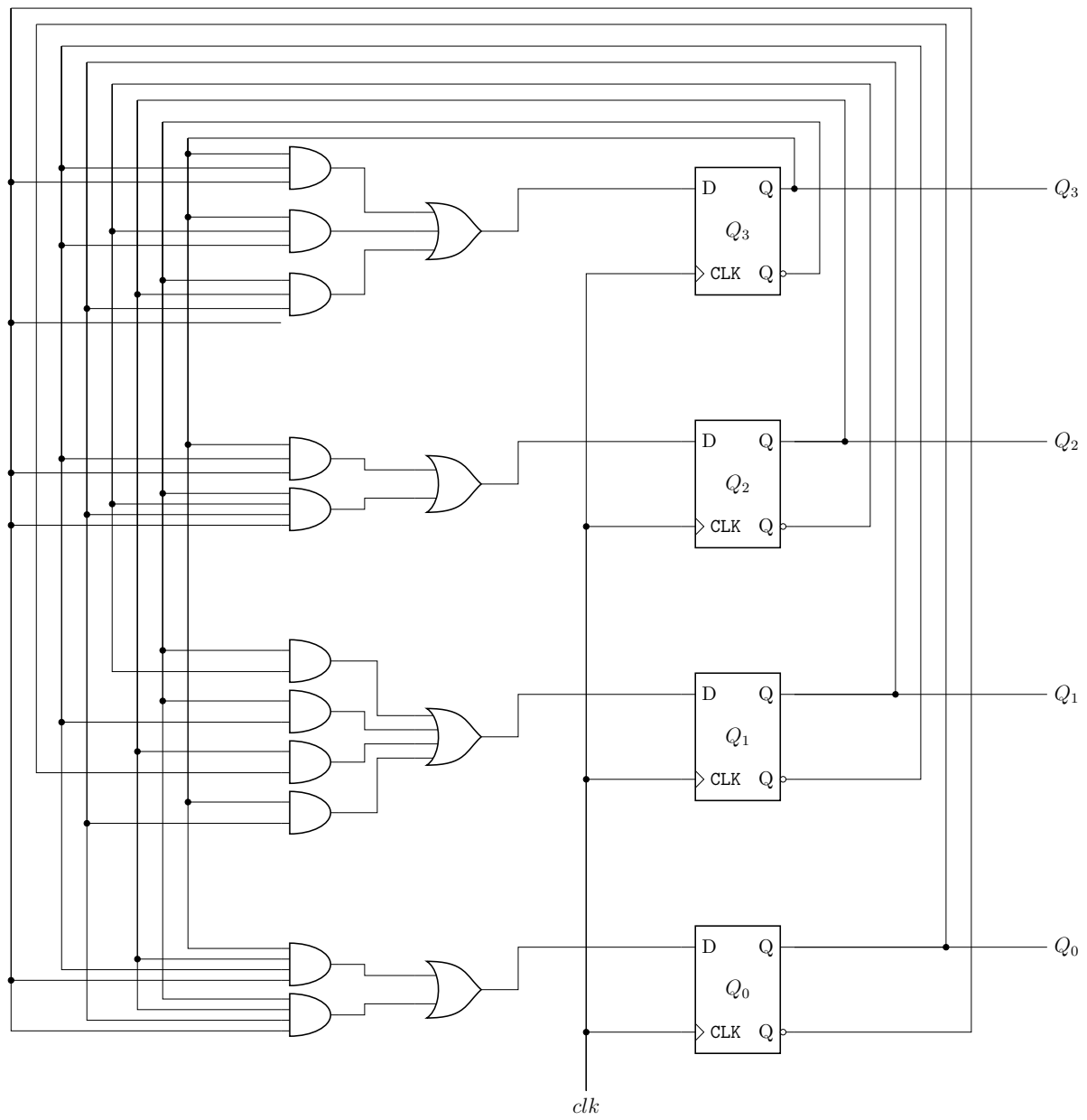Logic Diagram:

4.

With Don't Cares**State Table with TFF Inputs:**

Current State			Next State			TFF Inputs		
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	T_2	T_1	T_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	x	x	x	x	x	x
0	1	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0	0
1	0	1	x	x	x	x	x	x
1	1	0	1	0	0	0	1	0
1	1	1	1	1	0	0	0	1

Karnaugh Maps:

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	0	0	1	X
1	1	X	0	0

 T_2

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	0	1	0	X
1	0	X	0	1

 T_1

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	1	0	0	X
1	0	X	1	0

 T_0 **Simplified Boolean Expression:**

$$T_2 = Q_2'Q_1 + Q_2Q_1'$$

$$T_1 = Q_1'Q_0 + Q_1Q_0'$$

$$T_0 = Q_2'Q_0' + Q_2Q_0$$

In this case, the actual state table is:

Current State			Next State			TFF Inputs		
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	T_2	T_1	T_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	1	0	1	1	1	1
0	1	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0	0
1	0	1	0	1	0	1	1	1
1	1	0	1	0	0	0	1	0
1	1	1	1	1	0	0	0	1

As shown in the state table, the states with don't cares form a loop. Thus, the counter may not work properly.

Without Don't Cares

We can force the unused states go to the 000 state.

State Table with TFF Inputs:

Current State			Next State			TFF Inputs		
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	T_2	T_1	T_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	0	0	0	0	1	0
0	1	1	1	1	1	1	0	0
1	0	0	0	0	0	1	0	0
1	0	1	0	0	0	1	0	1
1	1	0	1	0	0	0	1	0
1	1	1	1	1	0	0	0	1

Karnaugh Maps:

Q_2	$Q_1 Q_0$			
	00	01	11	10
0	0	0	1	0
1	1	1	0	0

T_2

Q_2	$Q_1 Q_0$			
	00	01	11	10
0	0	1	0	1
1	0	0	0	1

T_1

$Q_1 Q_0 \backslash Q_2$	00	01	11	10
0	1	0	0	0
1	0	1	1	0

$$T_0$$

Simplified Boolean Expression:

$$T_2 = Q_2 Q_1' + Q_2' Q_1 Q_0$$

$$T_1 = Q_1 Q_0' + Q_2' Q_1' Q_0$$

$$T_0 = Q_2 Q_0 + Q_2' Q_1' Q_0'$$