

Digital Logic(H)

Southern University of Science and Technology

Mengxuan Wu

12212006

Theory Assignment 3

Mengxuan Wu

1.

State Equation:

$$A(t+1) = J_A A' + K'_A A = (Bx + B'y')A' + (B'xy')'A$$

$$B(t+1) = J_B B' + K'_B B = (A'x)B' + (A + xy)'B$$


Output Equation:

$$z = Ax'y' + Bx'y'$$

State Table:

Present State		Input		Next State		Output
<i>A</i>	<i>B</i>	<i>x</i>	<i>y</i>	<i>A</i>	<i>B</i>	<i>z</i>
0	0	0	0	1	0	0
0	0	0	1	0	0	0
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	1	0
1	0	0	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	0
1	0	1	1	1	0	0
1	1	0	0	1	0	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	0	0

State Diagram:

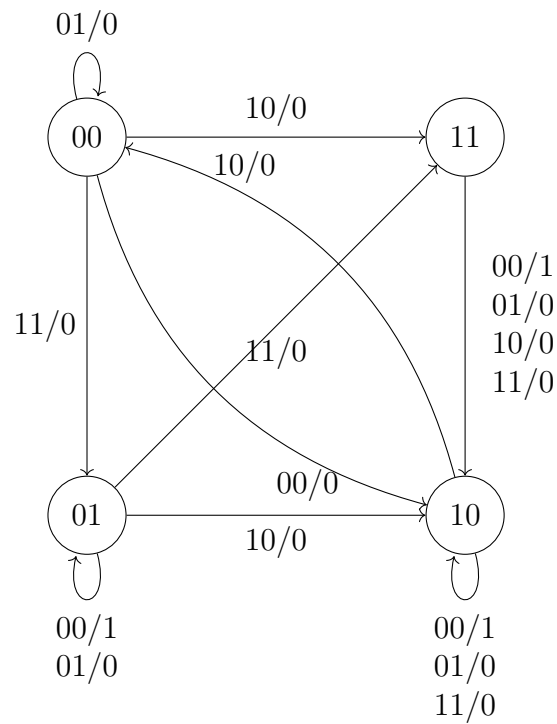

2.

Input Equation:

$$T_A = A + B$$

$$T_B = A' + B$$

Output Equation:


$$A(t+1) = A \oplus T_A = A \oplus (A + B)$$

$$B(t+1) = B \oplus T_B = B \oplus (A' + B)$$

State Table:

Present State		Next State	
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>
0	0	0	1
0	1	1	0
1	0	0	0
1	1	0	0

State Diagram:

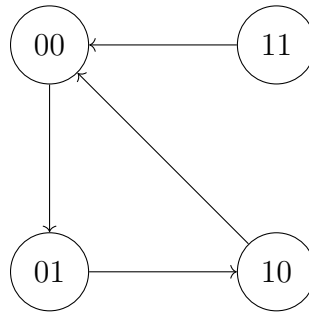

3.

a)

Input Equation:

$$J_1 = X$$

$$J_2 = X$$

$$K_1 = (XQ'_2)'$$

$$K_2 = (XQ_1)'$$

State Equation:

$$Q_1(t+1) = J_1Q'_1 + K'_1Q_1 = XQ'_1 + XQ_1Q'_2$$

$$Q_2(t+1) = J_2Q'_2 + K'_2Q_2 = XQ'_2 + XQ_1Q_2$$


Output Equation:

$$F = X \oplus Q'_2$$

State Table:

Present State		Input	Next State		Output
Q_1	Q_2	X	Q_1	Q_2	F
0	0	0	0	0	1
0	0	1	1	1	0
0	1	0	0	0	0
0	1	1	1	0	1
1	0	0	0	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	0	1	1


State Diagram:

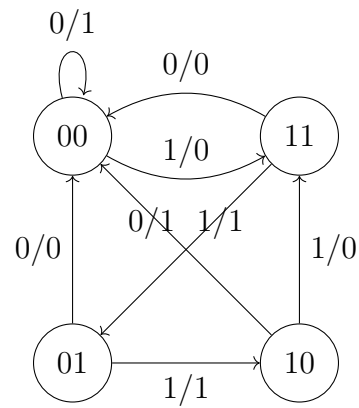

b)

This is a Mealy machine, because the output is determined by the input and the present state. For example, when the present state is 00, the output is different when the input is 0 or 1.

c)

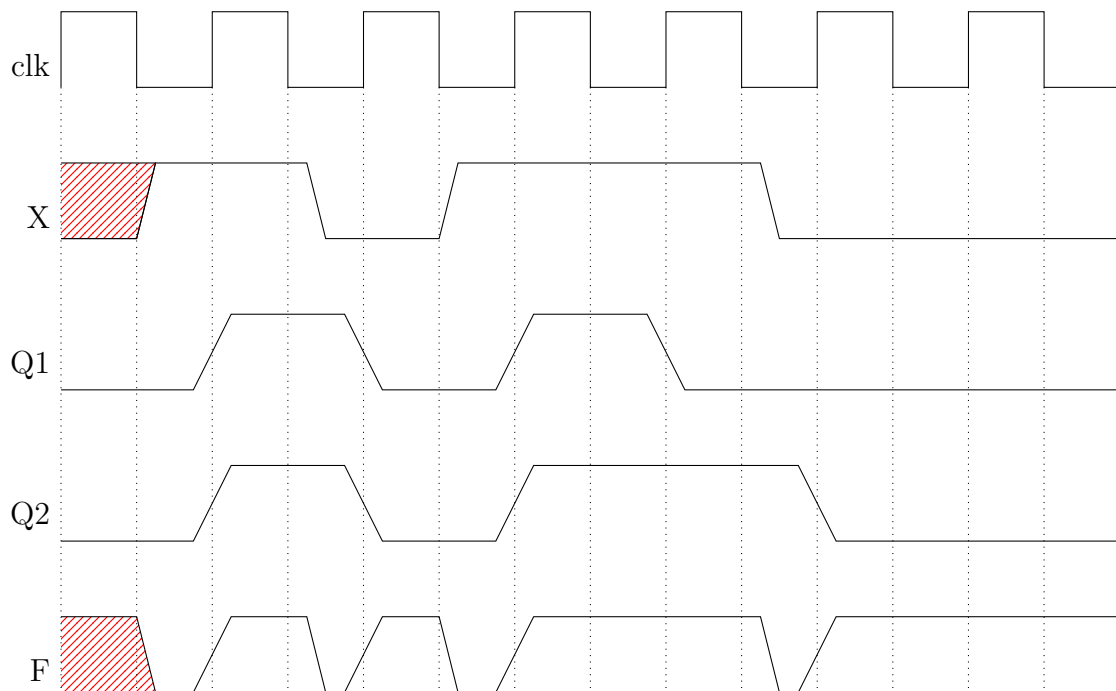

4.

State Table:

Present State	Input	Next State
Q	X	Q
a	0	b
a	1	a
b	0	d
b	1	c
c	0	d
c	1	c
d	0	a
d	1	d

Reduced State Table:

Present State	Input	Next State
Q	X	Q
a	0	b
a	1	a
b	0	d
b	1	b
d	0	a
d	1	d

Let $a = 00$, $b = 01$, $d = 10$, then the reduced state table is: **State Table with TFF**
Input:

Present State		Input	Next State		TFF Input	
Q_1	Q_2	X	Q_1	Q_2	T_1	T_2
0	0	0	0	1	0	1
0	0	1	0	0	0	0
0	1	0	1	0	1	1
0	1	1	0	1	0	0
1	0	0	0	0	1	0
1	0	1	1	0	0	0
1	1	0	X	X	X	X
1	1	1	X	X	X	X

Derive Input Equation:

		$Q_2 \backslash Q_1$			
		00	01	11	10
Q_1	0	0	0	0	1
	1	1	0	X	X

T_1

		$Q_2 \backslash Q_1$			
		00	01	11	10
Q_1	0	1	0	0	1
	1	0	0	X	X

T_2

$$T_1 = Q_1 X' + Q_2 X'$$

$$T_2 = Q_1' X'$$

5.


State Table:

Present State		Input		Next State
Q		En	D	Q
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
1	0	0	0	1
1	0	0	1	1
1	1	0	0	0
1	1	1	1	1

Derive Input Equation:

		$En \backslash Q$			
		00	01	11	10
Q	0	0	0	1	0
	1	1	1	1	0

$$Q(t+1) = EnD + QEn'$$

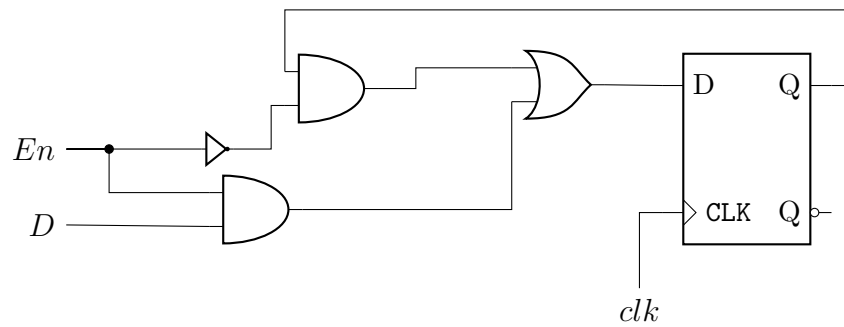Block Diagram:**6.****a)****Characteristic Table:**

A	B	$Q(t+1)$	Operation
0	0	0	Reset
0	1	$Q(t)$	No Change
1	0	$Q(t)'$	Complement
1	1	1	Set

b)**Characteristic Equation:**

$$Q(t+1) = A'BQ + AB'Q' + AB$$

State Table:

Current State	Input		Next State
Q	A	B	Q
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Simplify Characteristic Equation:

$Q \backslash AB$	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$Q(t+1) = Q'A + QB$$

c)

Excitation Table:

$Q(t)$	$Q(t+1)$	A	B	Operation
0	0	0	X	Reset
0	1	1	X	No Change
1	0	X	0	Complement
1	1	X	1	Set

d)

State Table with JKFF Input:

Current State		JKFF Input		Next State	New FF Input	
Q		J	K	Q	A	B
0	0	0	0	0	0	X
0	0	0	1	0	0	X
0	1	0	0	1	1	X
0	1	1	1	1	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	0	1	X	1
1	1	1	1	0	X	0

Simplify New FF Input:

$Q \backslash JK$	00	01	11	10
0	0	0	1	1
1	X	X	X	X

 A

$Q \backslash JK$	00	01	11	10
0	X	X	X	X
1	1	0	0	1


 B

The simplified JKFF input is:

$$A = J$$

$$B = K'$$

Block Diagram:

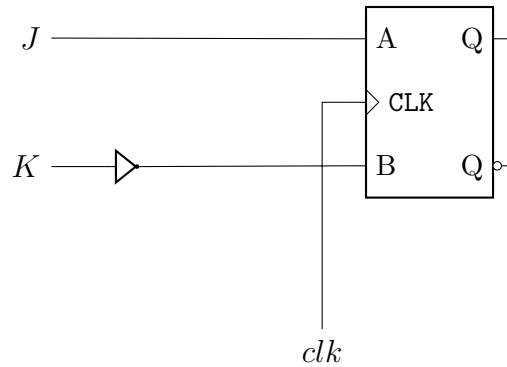


7.

Reduced State Table:

Present State	Next State		Output	
	$X = 0$	$X = 1$	$X = 0$	$X = 1$
a	f	b	0	0
b	d	a	0	0
d	g	a	1	0
f	f	b	1	1
g	g	d	0	1

State Diagram:

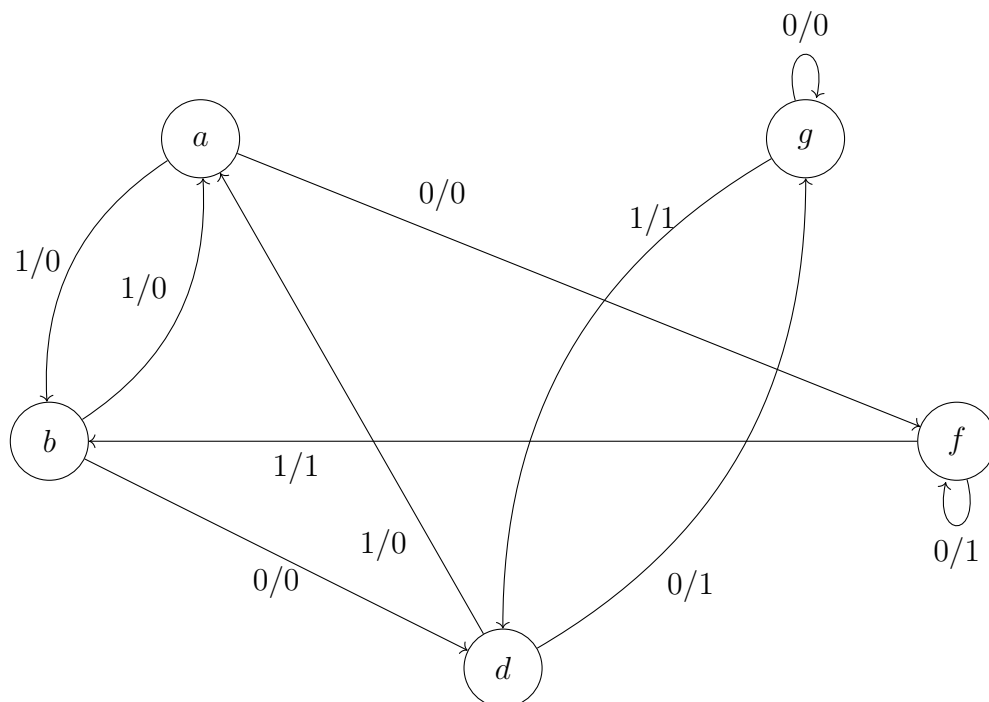

Let $a = 000$, $b = 001$, $d = 010$, $f = 011$, $g = 100$.

State Table with JKFF Input:

Present State			Input	Next State			JKFF Input						Output
Q_1	Q_2	Q_3	X	Q_1	Q_2	Q_3	J_1	K_1	J_2	K_2	J_3	K_3	F
0	0	0	0	0	1	1	0	X	1	X	1	X	0
0	0	0	1	0	0	1	0	X	0	X	1	X	0
0	0	1	0	0	1	0	0	X	1	X	X	1	0
0	0	1	1	0	0	0	0	X	0	X	X	1	0
0	1	0	0	1	0	0	1	X	X	1	0	X	1
0	1	0	1	0	0	0	0	X	X	1	0	X	0
0	1	1	0	0	1	1	0	X	X	0	X	0	1
0	1	1	1	0	0	1	0	X	X	1	X	0	1
1	0	0	0	1	0	0	X	0	0	X	0	X	0
1	0	0	1	0	1	0	X	1	1	X	0	X	1
1	0	1	0	X	X	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X

Simplify JKFF Input:

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	X	X	X	X
10	X	X	X	X

J_1

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	X	X	X	X
10	0	1	X	X

K_1

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	1	0	0	1
01	X	X	X	X
11	X	X	X	X
10	0	1	X	X

 J_2

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	X	X	X	X
01	1	1	1	0
11	X	X	X	X
10	X	X	X	X

 K_2

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	1	1	X	X
01	0	0	X	X
11	X	X	X	X
10	0	0	X	X

 J_3

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	X	X	1	1
01	X	X	0	0
11	X	X	X	X
10	X	X	X	X

 K_3


The simplified JKFF input is:

$$\begin{aligned}
 J_1 &= Q_2 Q'_3 X' \\
 J_2 &= Q'_1 X' + Q_1 X \\
 J_3 &= Q'_1 Q'_2
 \end{aligned}$$

$$\begin{aligned}
 K_1 &= X \\
 K_2 &= Q'_3 + X \\
 K_3 &= Q'_2
 \end{aligned}$$

8.

State Diagram:

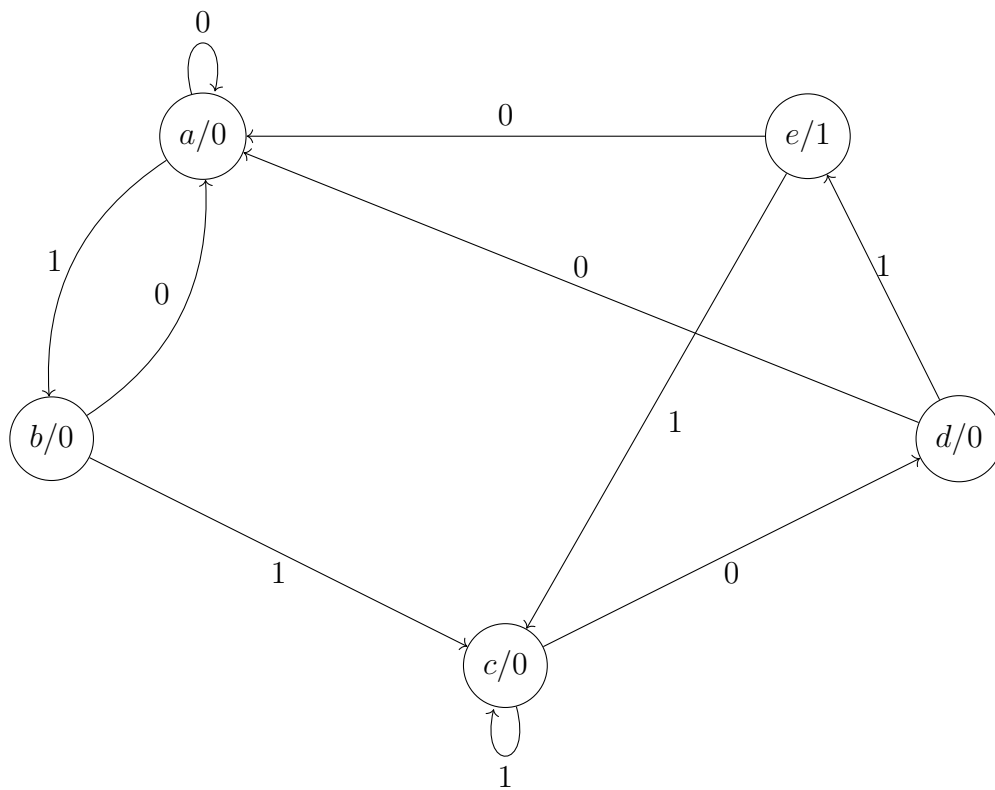Let $a = 000$, $b = 001$, $c = 010$, $d = 011$, $e = 100$.

State Table with DFF Input:

Present State			Input	Next State			DFF Input		
Q_1	Q_2	Q_3	X	Q_1	Q_2	Q_3	D_1	D_2	D_3
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0	1	0
0	1	0	0	0	1	1	0	1	1
0	1	0	1	0	1	0	0	1	0
0	1	1	0	0	0	0	0	0	0
0	1	1	1	1	0	0	1	0	0
1	0	0	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	1	0
1	0	1	0	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X

Simplify DFF Input:

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	0	0	X	X

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	0	0	1	0
01	1	1	0	0
11	X	X	X	X
10	0	1	X	X

$Q_3 \backslash Q_1 Q_2$	00	01	11	10
00	0	1	0	0
01	1	0	0	0
11	X	X	X	X
10	0	0	X	X

 D_1 D_2 D_3

The simplified DFF input is:

$$D_1 = Q_2 Q_3 X$$

$$D_2 = Q_2 Q_3' + Q_1 X + Q_2' Q_3 X$$

$$D_3 = Q_2 Q_3' X' + Q_1' Q_2' Q_3 X$$