



Verilog Assignment

- Continuous Assignment (Data flow Design)
- Procedural Assignment (Behavioral Design)
 - Blocking Assignment '='
 - Nonblocking Assignment '<='

Verilog Assignments

- Continuous Assignment (Dataflow Design)
 - LHS must be wire
- Procedural Assignment (Behavioral Design)
 - within always block
 - LHS must be reg

```
module some_circuit (  
    // inputs and outputs  
);
```

LHS

RHS

```
assign x = (a & b) | c;
```

Continuous

```
always @(*)  
begin
```

LHS

RHS

```
    y = (a & b) | c;
```

Procedural

```
end  
endmodule
```

Procedural Assignments

- Blocking assignment (=):
 - Executes sequentially, causing the next assignment to wait until the current assignment is completed.
- Nonblocking assignment (<=):
 - Executes concurrently, allowing multiple assignments to happen simultaneously without waiting for each other.

```
module some_circuit (  
    // inputs and outputs  
);
```

```
always @(*)  
begin
```

Blocking Assignment

```
    y = (a & b) | c;
```

```
end  
endmodule
```

```
module some_circuit (  
    // inputs and outputs  
);
```

```
always @(*)  
begin
```

Nonblocking Assignment

```
    y <= (a & b) | c;
```


```
end  
endmodule
```


Combinational logic + blocking



```
// Blocking assignments
always @(a, b, c)
begin
    x = a;
    x = x ^ b;
    x = x | c;
end
```

The order matters!

 


 


Combinational logic + nonblocking

```
// Nonblocking assignments  
always @(a, b, c)  
begin  
    x <= a;  
    x <= x ^ b;  
    x <= x | c;  
end
```

 non sense circuit
should not design like that




Sequential logic + blocking

 

```
// Blocking assignment
always @(posedge clk)
begin
    Q1 = D;
    Q2 = Q1;
end
```

 ➤ You must change code order to make it working properly




Sequential logic + nonblocking



```
// Nonblocking assignment  
always @(posedge clk)  
begin  
    Q1 <= D;  
    Q2 <= Q1;  
end
```

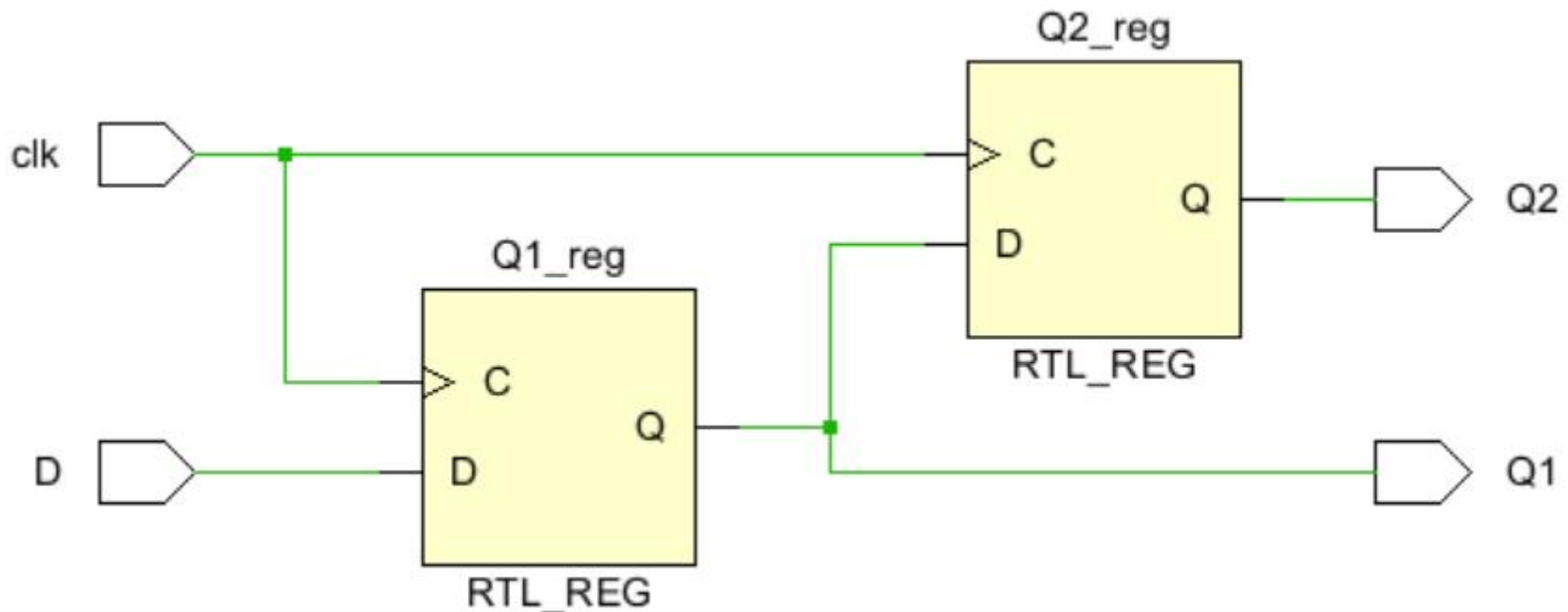shift register with 2
cascade DFFs
the order doesn't matter





Assignment suggestions

- Blocking assignments for combinational logic
 - continuous assignment
 - within always `@(*)` blocks.
- Nonblocking assignments for sequential logic
 - within always `@(posedge clk)`
 - or always `@(negedge clk)` blocks
- Don't mix blocking and nonblocking together within same always block