

DIGITAL LOGIC

Chapter 4 part2: Standard Components


2023 Fall

Today's Agenda

- Recap
- Context
 - Decoder
 - Multiplexer
 - Encoder
- Reading: Textbook, Chapter 4.9-4.11
 - Next Lecture we continue to chapter 5
 - Arithmetic Logic will be taught later



Recap

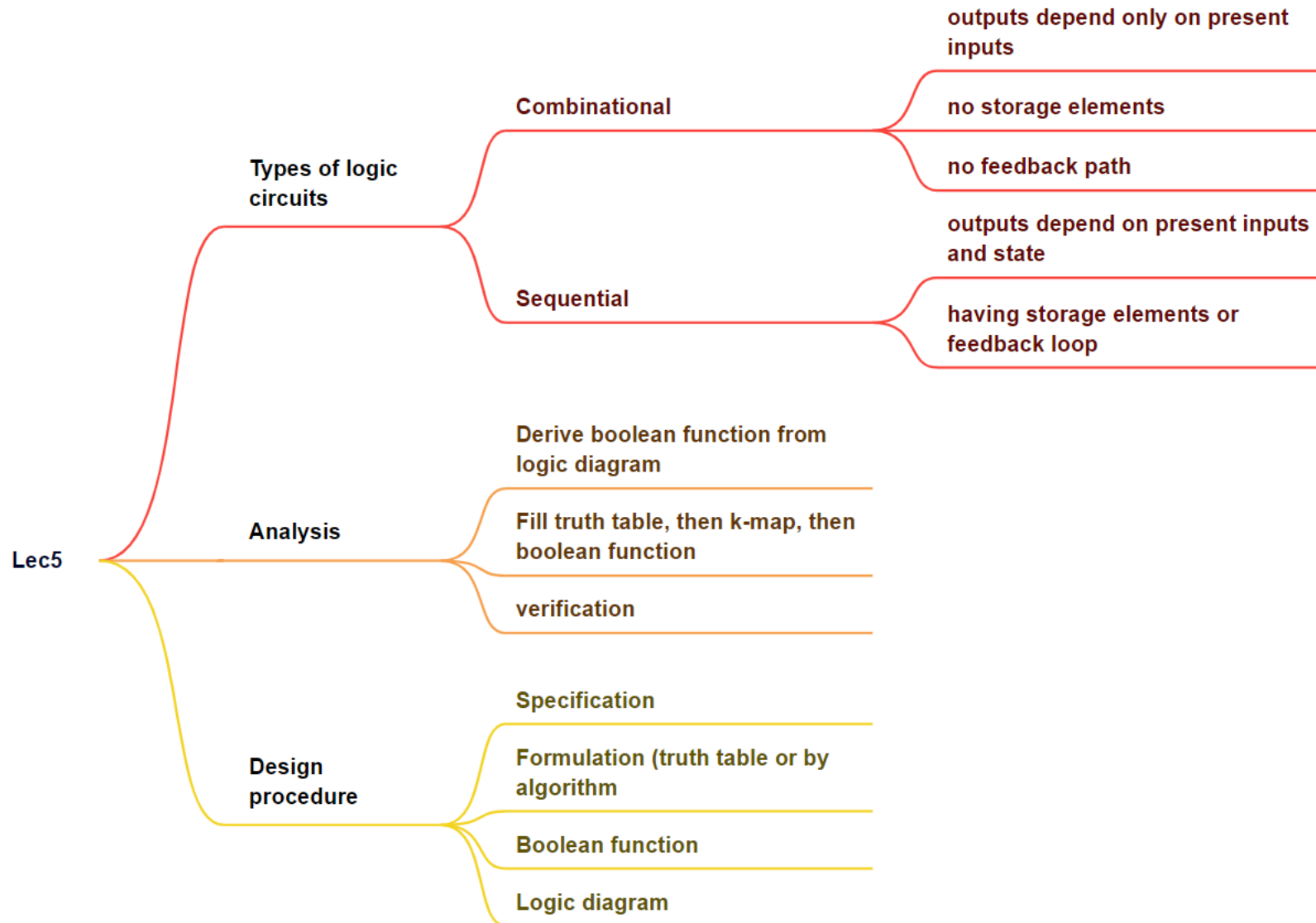



Outline

- **Decoder**
- Multiplexer
- Encoder
- Gate Behavior


One-hot Representation

- Represent a set of N elements with N bits
- Exactly one bit is set

| Binary | One-hot |
|--------|----------|
| 000 | 00000001 |
| 001 | 00000010 |
| 010 | 00000100 |
| 011 | 00001000 |
| 100 | 00010000 |
| 101 | 00100000 |
| 110 | 01000000 |
| 111 | 10000000 |

Decoder

- A decoder is a combinational circuit that converts binary information from n input lines to m (maximum of 2^n) unique output lines
 - n -to- m -line decoder
- A binary one-hot decoder converts a symbol from binary code to a one-hot code
 - Output variables are mutually exclusive because only one output can be equal to 1 at any time (the 1-minterm)
- Example
 - binary input a to one-hot output b
 - $b[i] = 1$ if $a = i$ or $b = 1 \ll a$
 - a stands for position of 1 in b

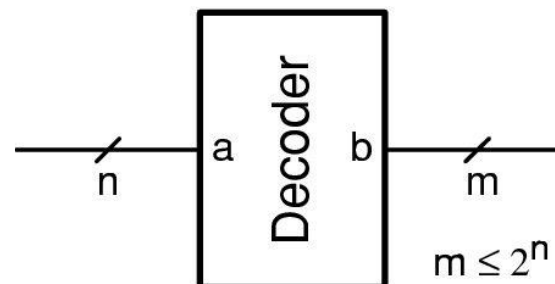

1-to-2-Line Decoder

- Step1: Specification
- Step2: Formulation

| x | D ₁ | D ₀ |
|---|----------------|----------------|
| 0 | 0 | 1 |
| 1 | 1 | 0 |


- Step3: Optimization

$$D_0 = x'$$

$$D_1 = x$$

minterms

- Step4: Logic Diagram

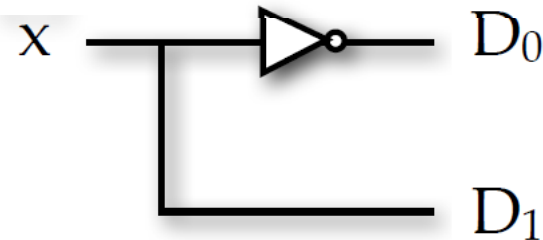


2-to-4-Line Decoder

Step 1,2

| a_1 | a_0 | b_3 | b_2 | b_1 | b_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 |


Step 3
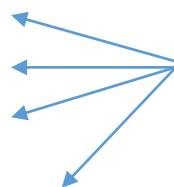
$$\begin{aligned} b_3 &= a_1 a_0 \\ b_2 &= a_1 a_0' \\ b_1 &= a_1' a_0 \\ b_0 &= a_1' a_0' \end{aligned}$$



minterms

Step 4

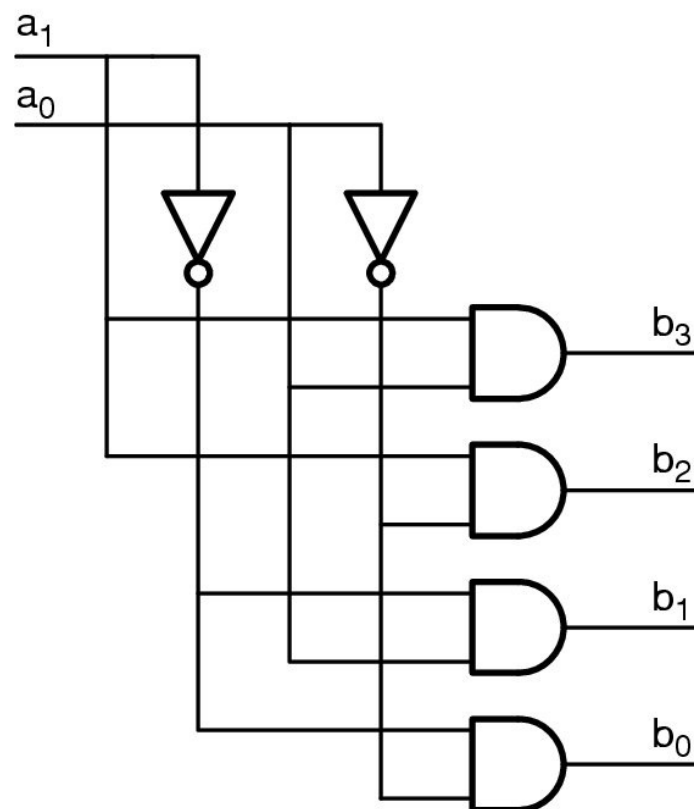


3-to-8-Line Decoder

- Each output of the decoder represents one of the eight minterms of the Boolean function

Step 1,2

| Inputs | | | Outputs | | | | | | | |
|--------|-----|-----|---------|-------|-------|-------|-------|-------|-------|-------|
| x | y | z | D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |



Step 4

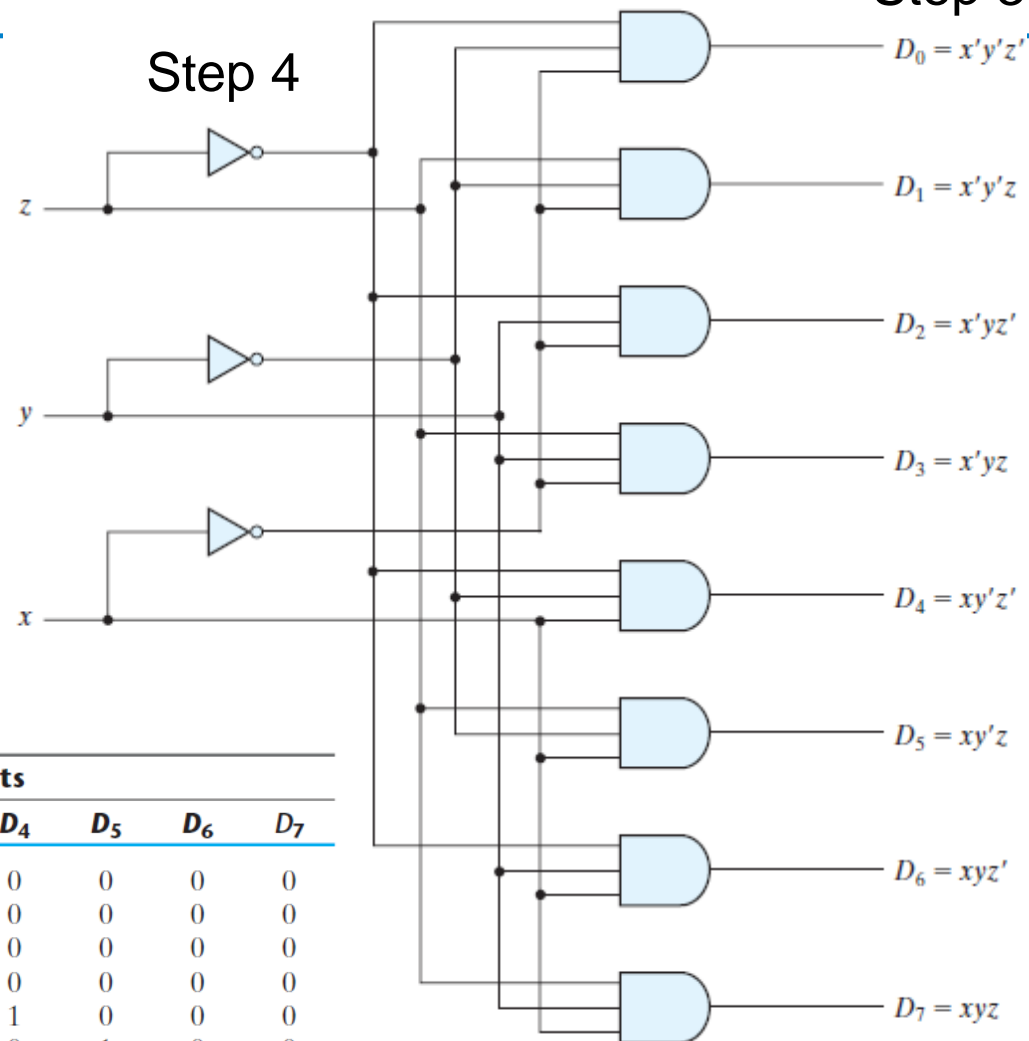

Step 3

Logic Diagram vs Block Diagram

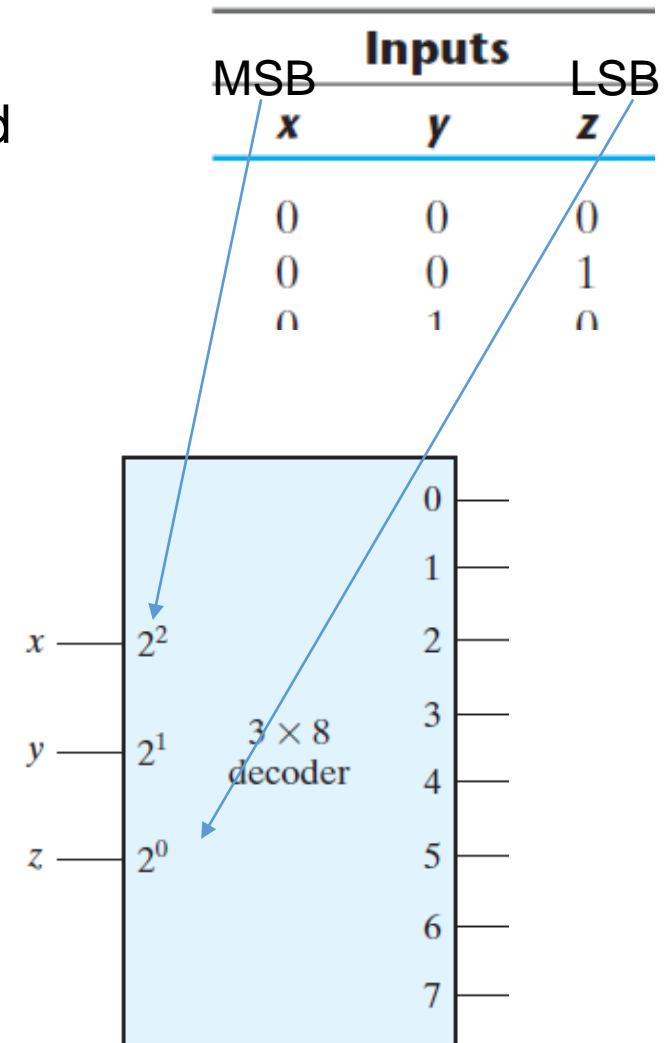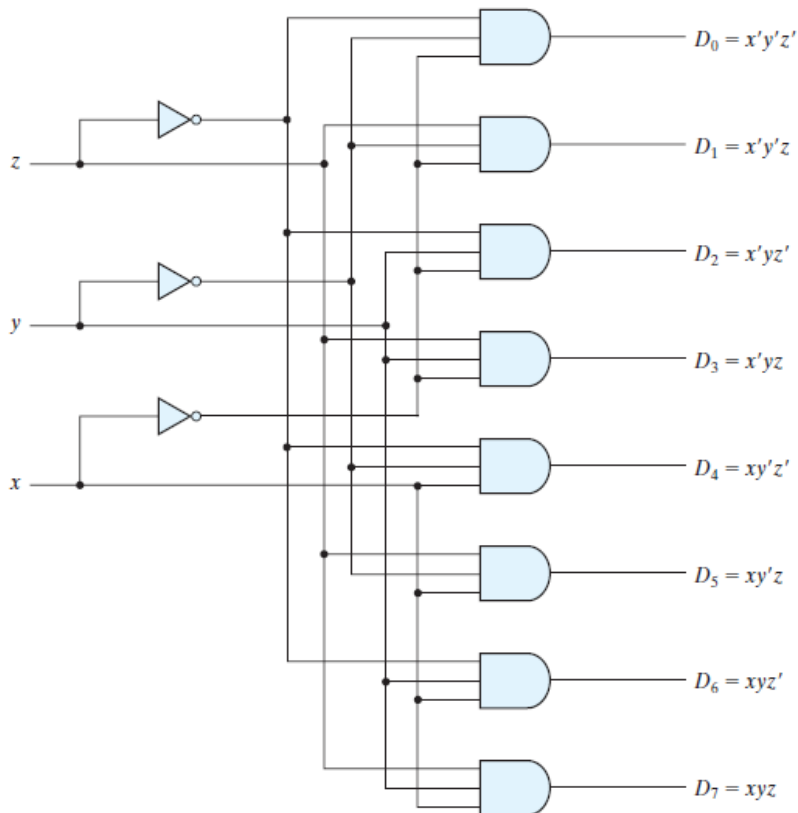- We can use block diagram
 - Clearly denoting the input position and output sequence



Main Usages of Decoders

- Minterm generator (最小项生成器):
 - Generate the 2^n (or fewer) minterms of n input variables. For example: a 3-8 line decoder
- Data demultiplexing (数据分配器):
 - A decoder with enable input can function as a **demultiplexer** – a circuit that receives information from a single line and directs it to one of 2^n possible output lines.
- Display decoding: (显示解码)
 - Decoders are used in display systems to select a specific output line based on the input code and drive the corresponding segment of the display.
- Address decoding: (地址解码):
 - Identify a memory cell, disk sector, or other memory or storage device, to ensure one device can communicate with the processor at one time.

Decoder for logic implementation


Example1

- Decoder can be used to implement the logic function by connecting the appropriate minterms to an OR gate.
 - Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n decoder in conjunction with m external OR gates

| x | y | z | C | S |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

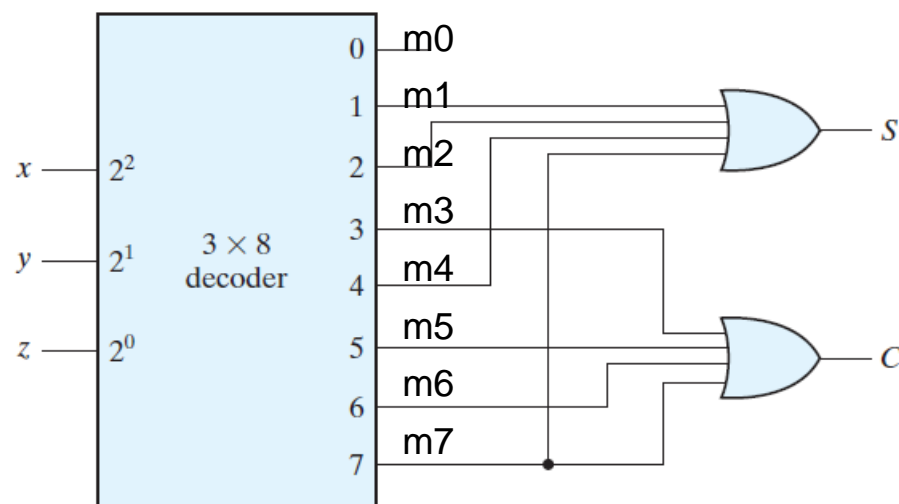


Decoder for logic implementation

Example2

- Exercise:
 - Implement $Y = A \text{ XNOR } B$ using a 2-to-4 line decoder and external OR gate, you need to clearly write down the input and output pins

$$\begin{aligned} Y &= A \text{ XNOR } B \\ &= (A \oplus B)' \\ &= A'B' + AB \\ &= \sum(0, 3) \end{aligned}$$


Connect output 0 and 3
to an OR gate

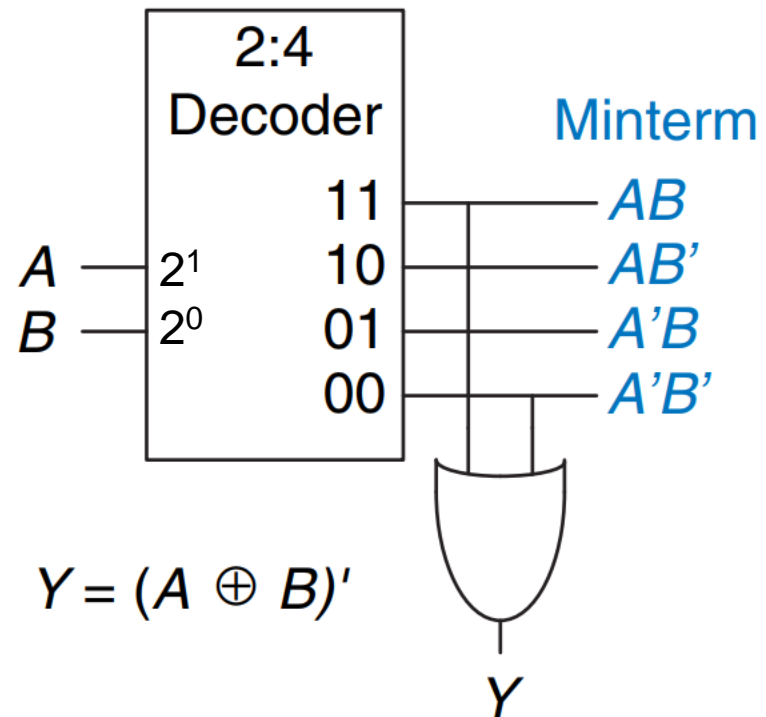

Decoder for logic implementation

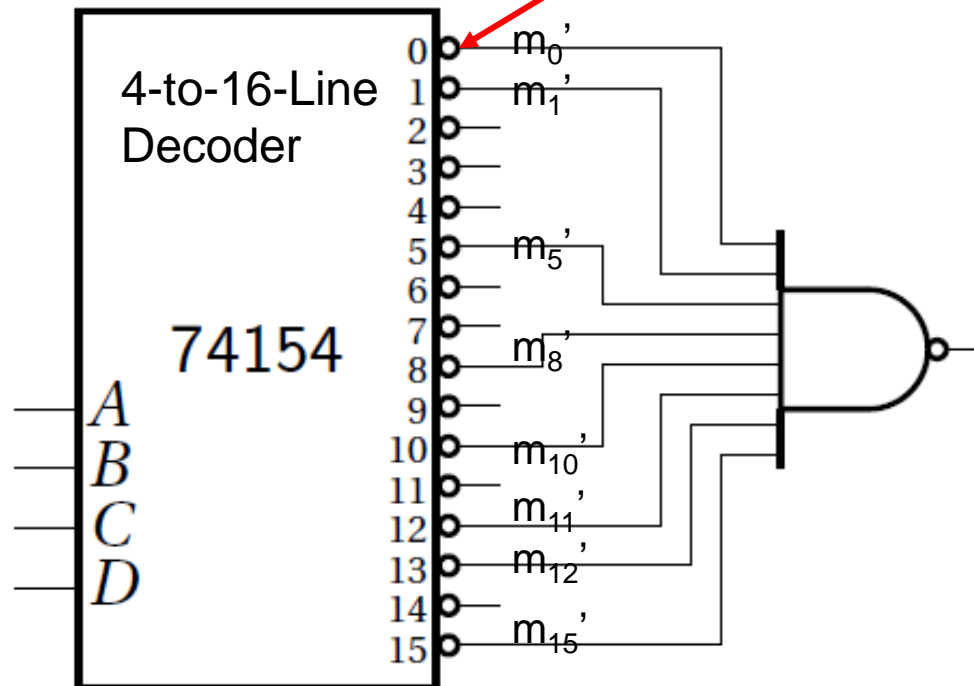
Example3

- MSI 74154: 4-to-16 line decoder
 - If $A = B = C = D = 0$ the output 0 of the decoder is **0** while all other outputs are 1. (**active low**) → generate inverse of minterms
 - Example: $F(A,B,C,D) = \sum(0, 1, 5, 8, 10, 12, 13, 15)$.
$$= [(m_0 + m_1 + m_5 + m_8 + m_{10} + m_{12} + m_{13} + m_{15})]'$$
$$= (m_0' \cdot m_1' \cdot m_5' \cdot m_8' \cdot m_{10}' \cdot m_{12}' \cdot m_{13}' \cdot m_{15}')$$



Enabling

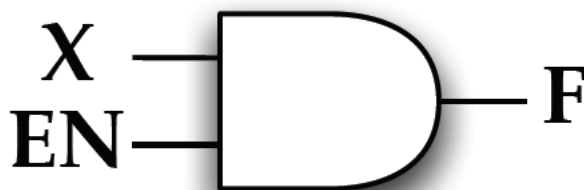- Enabling permits an input signal to pass through to an output.



- $F = EN \cdot X$


| EN | X | F |
|----|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Decoder with Enable Input

- Decoder with enable control (E)

Step1,2


| | E | A ₀ | C ₁ | C ₀ |
|--------------------|---|----------------|----------------|----------------|
| Active High Enable | 1 | 0 | 0 | 1 |
| | 1 | 1 | 1 | 0 |
| Low → disabled | 0 | X | 0 | 0 |

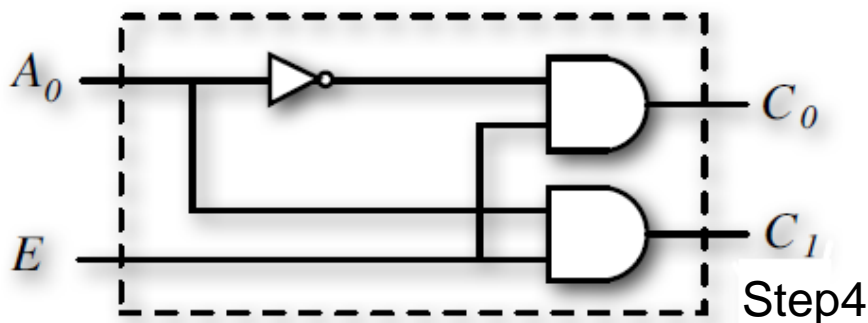

Step3

$$C_0 = EA_0'$$

$$C_1 = EA_0$$

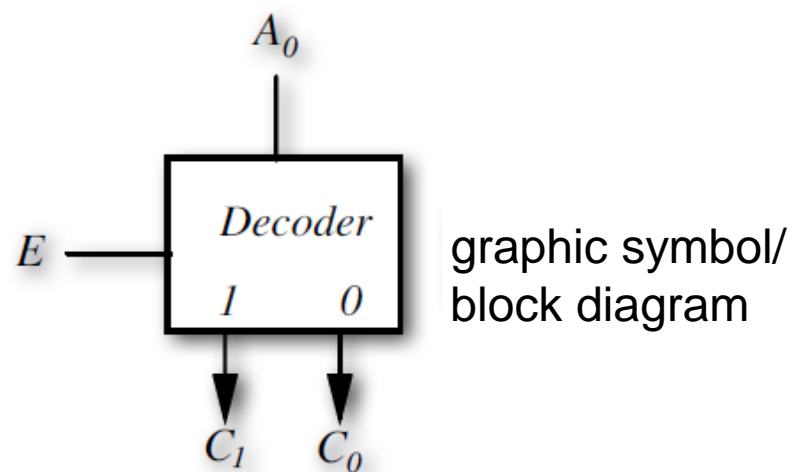


1-2 Line Decoder with Enable

Decoder with Active-Low Enable

- Constructed with NAND gates
 - decoder minterms in their complemented form (more economical)

| | <i>E</i> | <i>A</i> | <i>B</i> | <i>D</i> ₀ | <i>D</i> ₁ | <i>D</i> ₂ | <i>D</i> ₃ |
|-------------------|----------|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|
| High → disabled | 1 | <i>X</i> | <i>X</i> | 1 | 1 | 1 | 1 |
| Active Low Enable | 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| | 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| | 0 | 1 | 1 | 1 | 1 | 1 | 0 |

Output in complement form

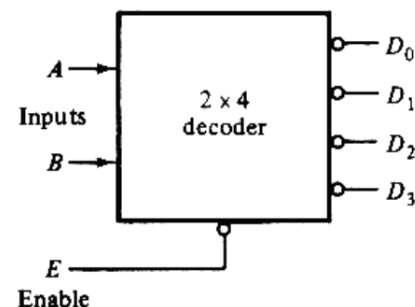


$$D_0 = (E'A'B)'$$

$$D_1 = (E'A'B')$$


$$D_2 = (E'AB)'$$

$$D_3 = (E'AB')$$

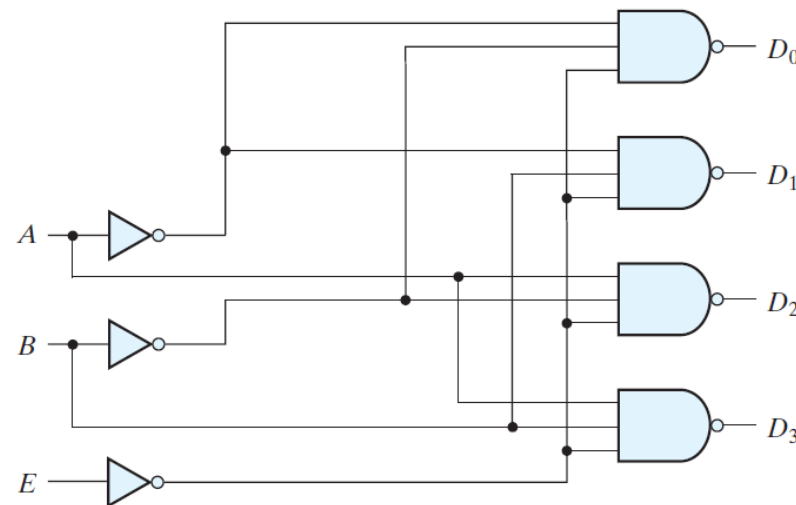

Decoder Expansion

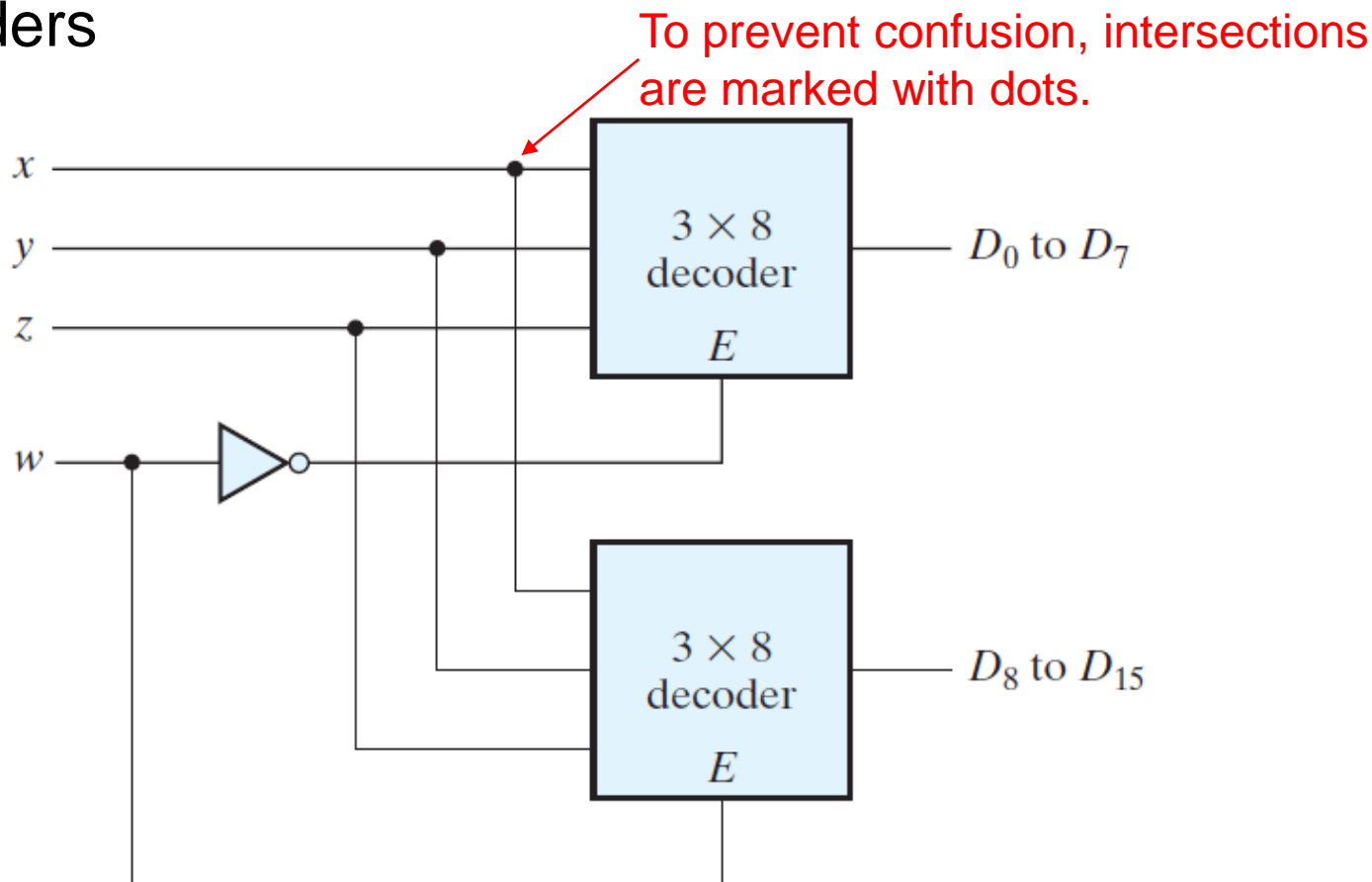
- Larger decoders can be implemented with smaller decoders




A 4-to-16-line decoder from two 3-to-8-line decoders

Other Decoders

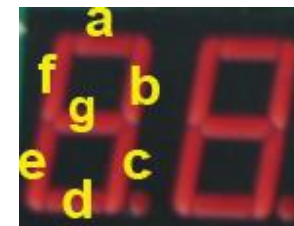- BCD-to-7-Segment Display Decoder
 - input (ABCD), output (abcdefg)(MSB to LSB)
 - ABCD:0000~1001(0~9)



| BCD Input | | | | 7-Segment Display | | | | | | |
|------------------|---|---|---|-------------------|---|---|---|---|---|---|
| A | B | C | D | a | b | c | d | e | f | g |
| 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| All other inputs | | | | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

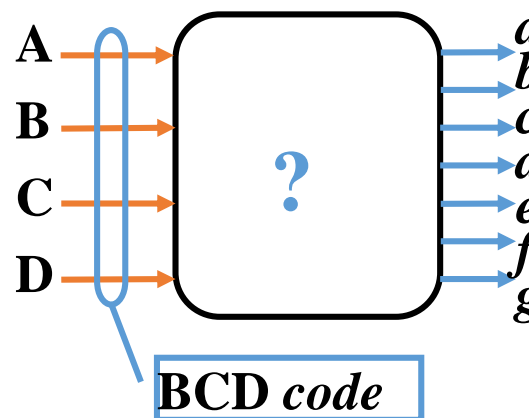

$$a = A'C + A'BD + B'C'D' + A'B'C'$$

$$b = A'B' + A'C'D' + A'CD + AB'C'$$

$$c = A'B + A'D + B'C'D' + AB'C'$$

$$d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$$

$$e = A'CD' + B'C'D'$$

$$f = A'BC' + A'C'D' + A'BD' + AB'C'$$

$$g = A'CD' + A'B'C + A'BC' + AB'C'$$





Outline

- Decoder
- **Multiplexer**
- Encoder
- Gate Behavior

Multiplexers (MUX)

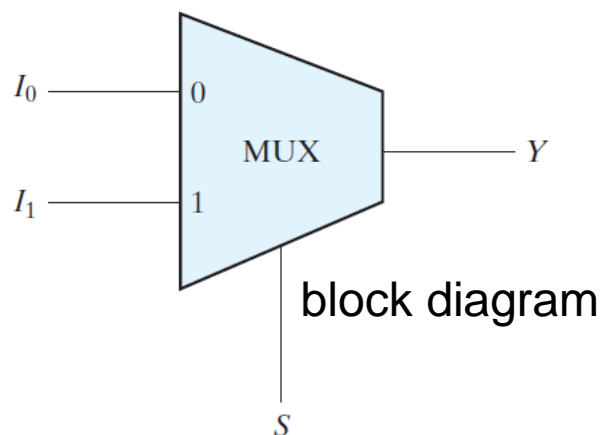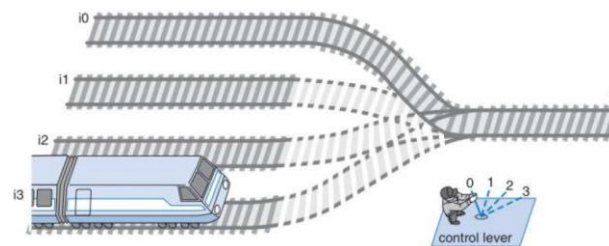- A Multiplexer selects (usually by n select lines) binary information from one of many (usually 2^n) input lines and directs it to a single output line.




Function table

| S | Y |
|---|-------|
| 0 | I_0 |
| 1 | I_1 |

Logic equation


$$Y = S'I_0 + SI_1$$

2:1 multiplexer

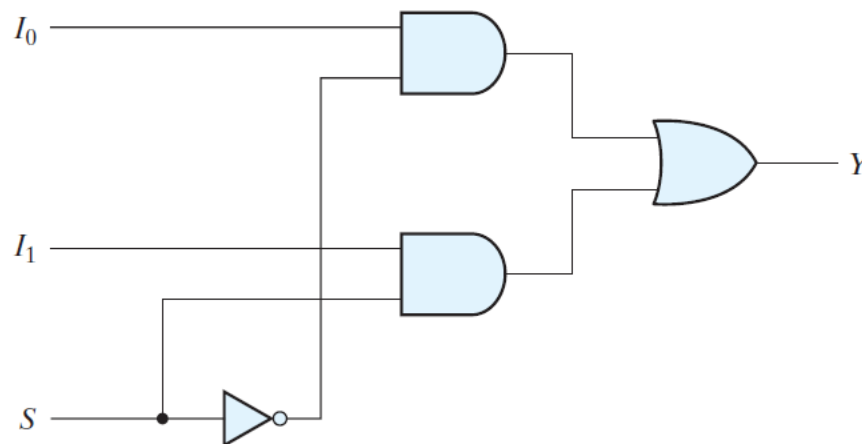


function table lists the input that is passed to the output for each combination of the binary selection values

4:1 MUX

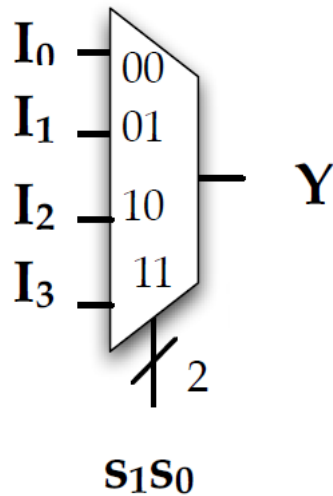

Function table

| S_1 | S_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |

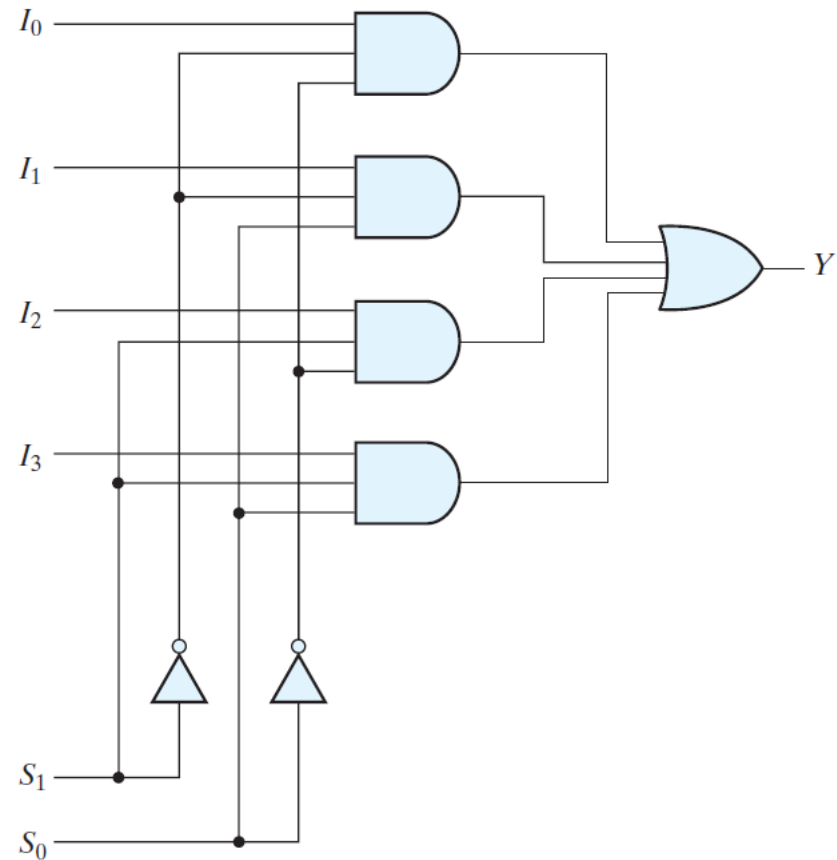


Logic equation

$$Y = s_1's_0'I_0 + s_1's_0I_1 + s_1s_0'I_2 + s_1s_0I_3$$

MUX Composition

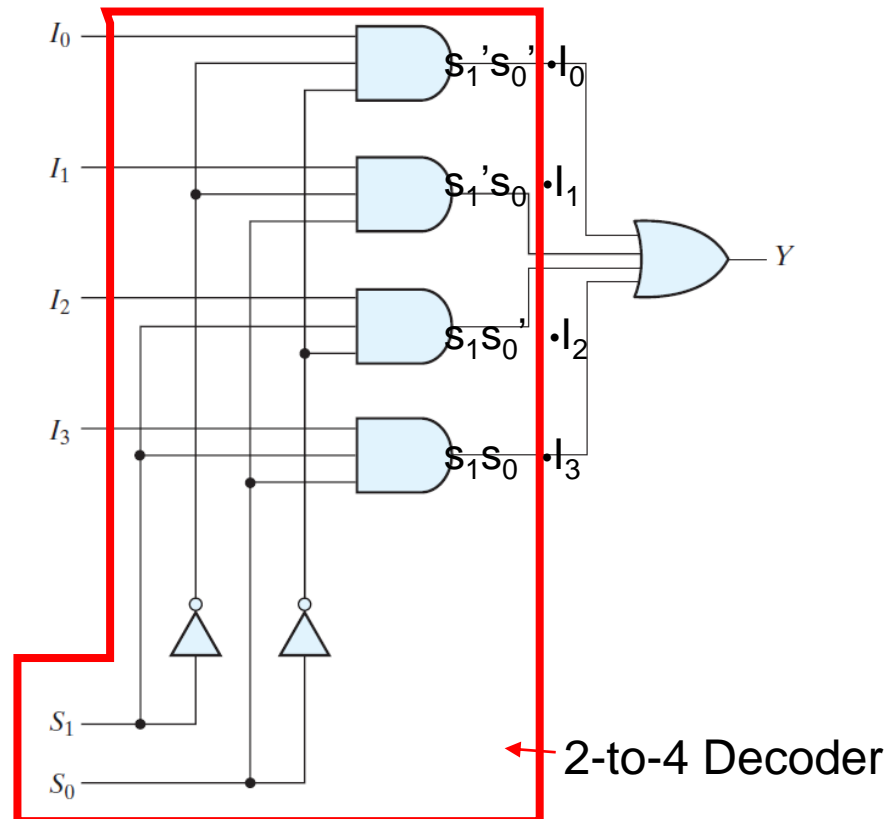- MUX = decoder + OR gate
 - The device has two control or selection lines S_1 and S_0 ,
 - Logic equation: $Y = s_1's_0'I_0 + s_1's_0I_1 + s_1s_0'I_2 + s_1s_0I_3$




MUX for logic implementation

Example1

- Implement AND function using MUX
 - can be used as a look-up table
 - 4:1 multiplexer can be used (truth table)

| A | B | Y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |


$Y = AB$

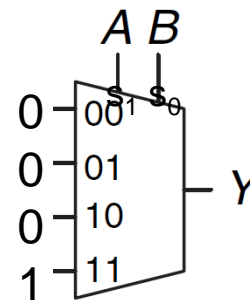

Exercise: Implement XNOR function using

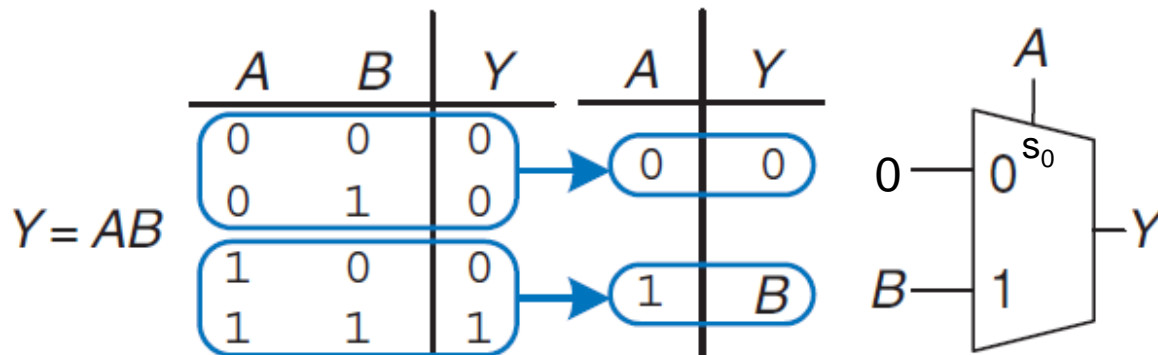- 1) a 4:1 MUX
- 2) a 2:1 MUX

- What if only 2:1 MUX is allowed to use?
 - By using variable as data inputs




MUX for logic implementation

Example2


- Implement the function $Y(A,B,C) = \sum(0,3,4,5)$ with MUX

1. using 8:1 MUX

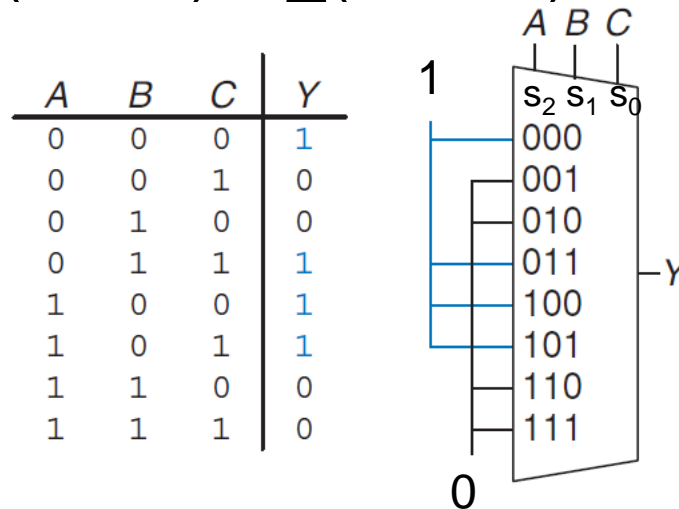

 2. using 4:1 MUX

- We can use 4:1 MUX by reducing the truth table to four rows by letting A,B as select bit s_1 and s_0



MUX for logic implementation


Example2

- Implement the function $Y(A,B,C) = \sum(0,3,4,5)$ with MUX
- 3. Using 2:1 MUX?

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

$Y = (B \oplus C)'$

$Y = B'$

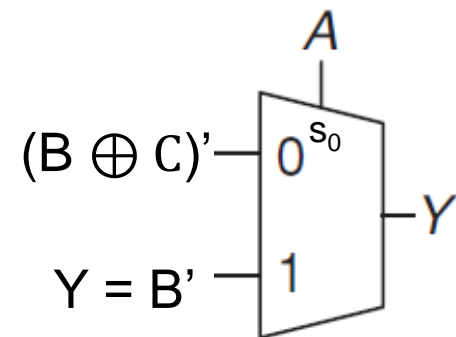


MUX for logic implementation

Example3

- Implement $F(A, B, C, D) = (1, 3, 4, 11, 12, 13, 14, 15)$ with three selection inputs Multiplexer.
 - A must be connected to selection input S_2 so that A, B, and C correspond to selection inputs S_2, S_1 , and S_0 , respectively


| A | B | C | D | F | |
|---|---|---|---|---|----------|
| 0 | 0 | 0 | 0 | 0 | $F = D$ |
| 0 | 0 | 0 | 1 | 1 | |
| 0 | 0 | 1 | 0 | 0 | $F = D$ |
| 0 | 0 | 1 | 1 | 1 | |
| 0 | 1 | 0 | 0 | 1 | $F = D'$ |
| 0 | 1 | 0 | 1 | 0 | |
| 0 | 1 | 1 | 0 | 0 | $F = 0$ |
| 0 | 1 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 0 | 0 | $F = 0$ |
| 1 | 0 | 0 | 1 | 0 | |
| 1 | 0 | 1 | 0 | 0 | $F = D$ |
| 1 | 0 | 1 | 1 | 1 | |
| 1 | 1 | 0 | 0 | 1 | $F = 1$ |
| 1 | 1 | 0 | 1 | 1 | |
| 1 | 1 | 1 | 0 | 1 | $F = 1$ |
| 1 | 1 | 1 | 1 | 1 | |

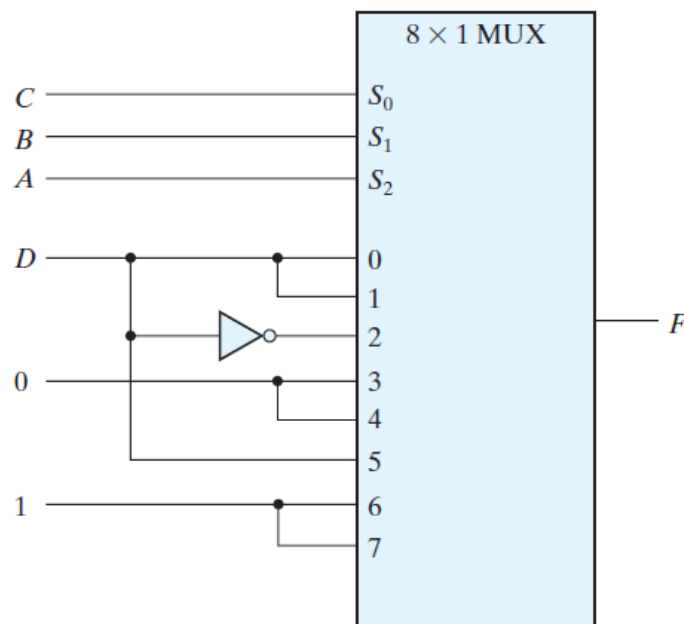


Quadruple 2:1 MUX (4-bit 2:1 MUX)

| E | S | Output Y |
|-----|-----|------------|
| 1 | X | all 0's |
| 0 | 0 | select A |
| 0 | 1 | select B |

Function table

 

four 2:1 MUX with enable

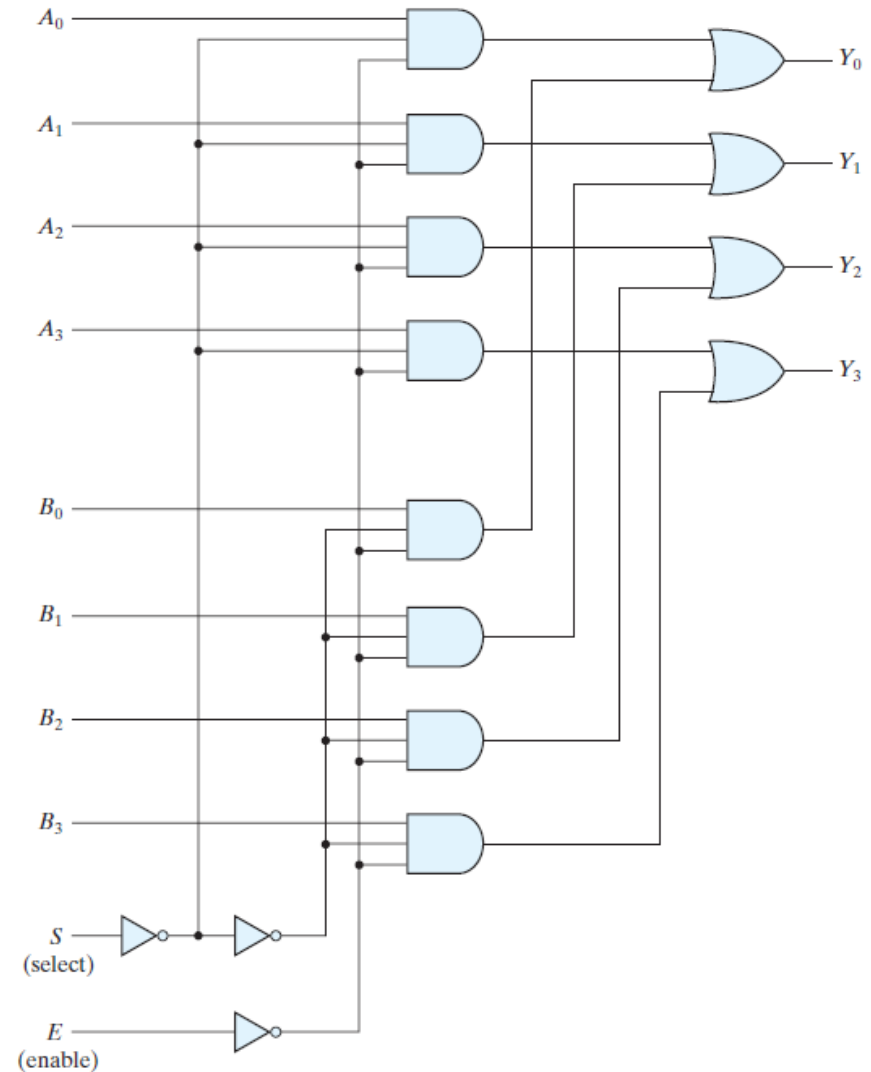

MUX Expansion

- Wider multiplexers, such as 8:1 and 16:1 multiplexers, can be built with smaller multiplexers

Function table


| S_1 | S_0 | Y |
|-------|-------|-------|
| 0 | 0 | D_0 |
| 0 | 1 | D_1 |
| 1 | 0 | D_2 |
| 1 | 1 | D_3 |

$f_1 = S_0'D_0 + S_0D_1$
 $f_2 = S_0'D_2 + S_0D_3$

Logic equation

$$\begin{aligned}
 Y &= s_1'f_1 + s_1f_2 \\
 &= s_1'(s_0'D_0 + s_0D_1) + s_1(s_0'D_2 + s_0D_3) \\
 &= s_1's_0'D_0 + s_1's_0D_1 + s_1s_0'D_2 + s_1s_0D_3
 \end{aligned}$$


4:1 MUX with three 2:1 MUX

 

MUX Expansion



- How to build a 16-to-1 multiplexer using five 4-to-1 multiplexers?
 - $16 = 2^4$
 - 4 bits for selection

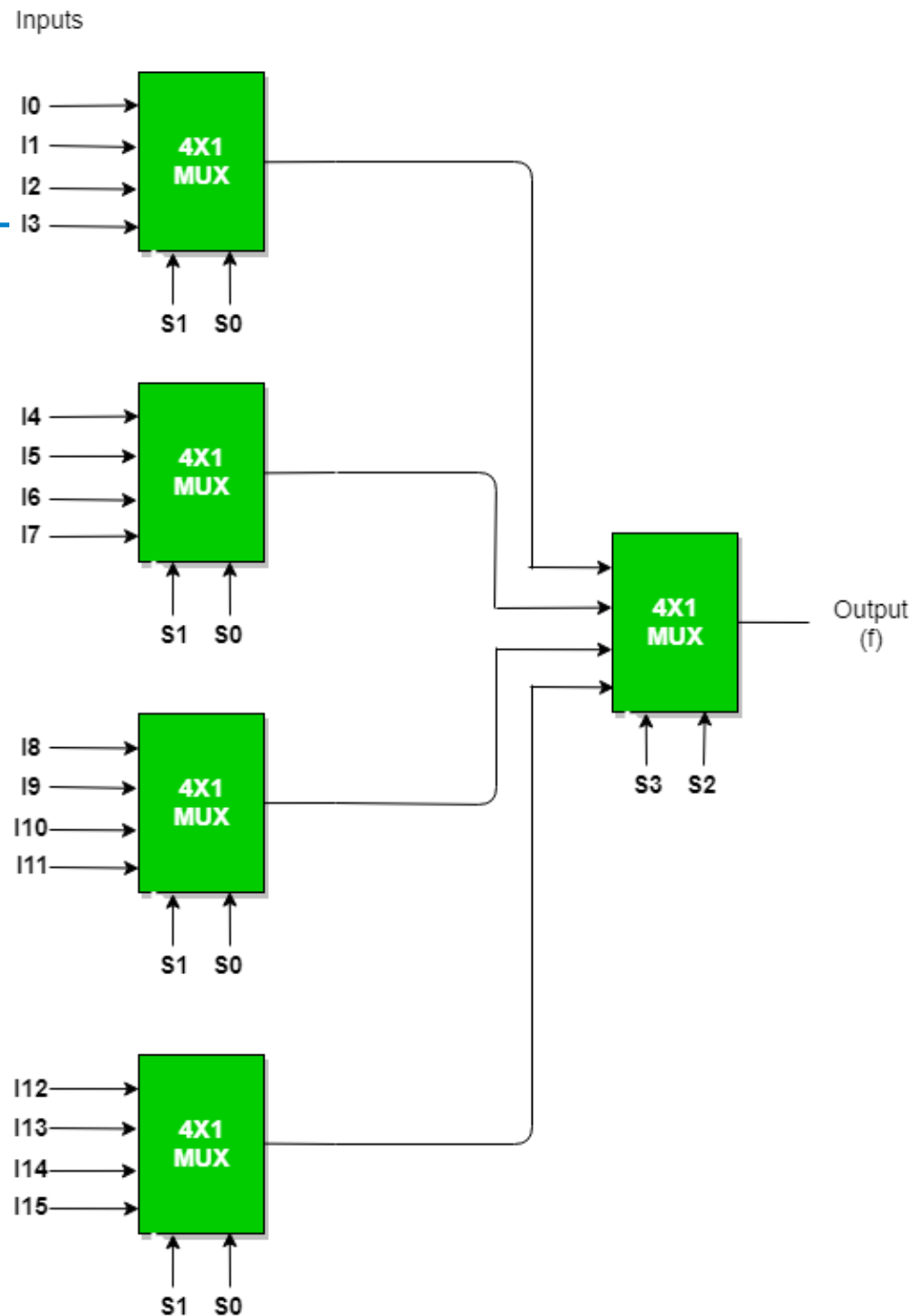Exercise: How to build a 8-to-1 multiplexer using two 4-to-1 MUX and a 2-to-1 MUX? You must carefully connect the selection and input pins



Demultiplexer

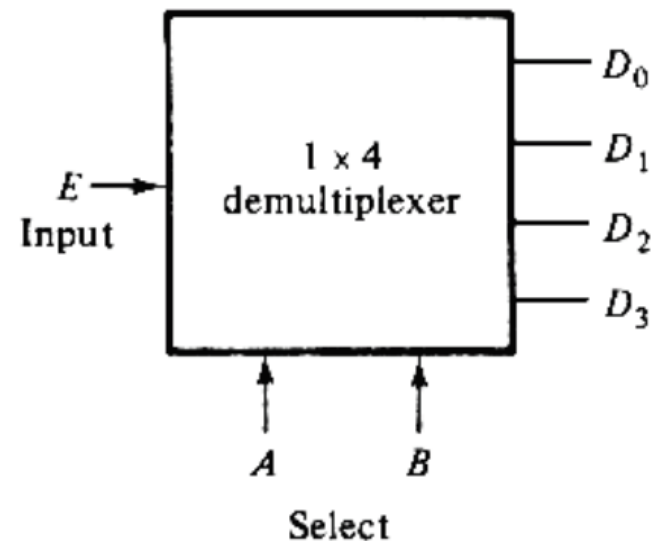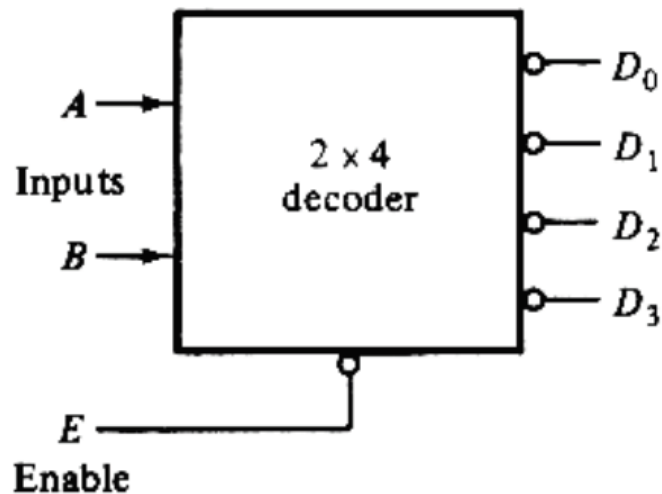- A decoder with enable input can function as demultiplexer
 - a circuit that receives information from a single line and directs it to one of 2^n possible output lines.
 - Because decoder and demultiplexer operations are obtained from the same circuit, a decoder with an enable input is referred to as a demultiplexer.




Outline

- Decoder
- Multiplexer
- **Encoder**
- Gate Behavior

Encoder

- An encoder is an inverse of a decoder
- Encoder is a logic module that converts a **one-hot** input signal to a binary-encoded output signal
- Other input patterns are **forbidden** in the truth table
- Example: a 4-→2 encoder

| a_3 | a_2 | a_1 | a_0 | b_1 | b_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |

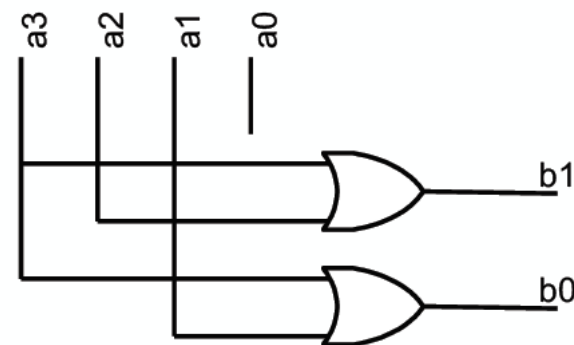

$$b_0 = a_3 + a_1$$

$$b_1 = a_3 + a_2$$

Encoder

- A combinational logic that performs the inverse operation of a decoder
 - Only one input has value 1 at any given time
 - Can be implemented with OR gates
- However, when both D3 and D6 goes 1, the output will be 111 (ambiguity)! **illegal inputs !Use priority encoder!**

| Inputs | | | | | | | | Outputs | | |
|--------|-------|-------|-------|-------|-------|-------|-------|---------|-----|-----|
| D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 | x | y | z |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |

$$x = D_4 + D_5 + D_6 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$z = D_1 + D_3 + D_5 + D_7$$

Priority Encoder

- Ensure only one of the input is encoded
- Assuming D_3 has the highest priority, while D_0 has the lowest priority.
- X is the don't care conditions, V is the valid output indicator.

| Inputs | | | | Outputs | | |
|--------|-------|-------|-------|---------|-----|-----|
| D_0 | D_1 | D_2 | D_3 | x | y | V |
| 0 | 0 | 0 | 0 | X | X | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| X | 1 | 0 | 0 | 0 | 1 | 1 |
| X | X | 1 | 0 | 1 | 0 | 1 |
| X | X | X | 1 | 1 | 1 | 1 |

$$V = D_0 + D_1 + D_2 + D_3$$

Priority Encoder

| D_0D_1 | | D_2D_3 | | | |
|----------|----|------------|---------------|---------------|---------------|
| | | 00 | 01 | 11 | 10 |
| D_0 | 00 | m_0 X | m_1 1 | m_3 1 | m_2 1 |
| | 01 | m_4 | m_5 1 | m_7 1 | m_6 1 |
| | 11 | m_{12} | m_{13} 1 | m_{15} 1 | m_{14} 1 |
| | 10 | m_8 | m_9 1 | m_{11} 1 | m_{10} X |

$x = D_2 + D_3$


$$x = D_2 + D_3$$

$$y = D_3 + D_1 D_2'$$

$$V = D_0 + D_1 + D_2 + D_3$$

| D_0D_1 | | D_2D_3 | | | |
|----------|----|---------------|---------------|---------------|----------|
| | | 00 | 01 | 11 | 10 |
| D_0 | 00 | m_0 X | m_1 1 | m_3 1 | m_2 |
| | 01 | m_4 1 | m_5 1 | m_7 1 | m_6 |
| | 11 | m_{12} 1 | m_{13} 1 | m_{15} 1 | m_{14} |
| | 10 | m_8 | m_9 1 | m_{11} 1 | m_{10} |

$y = D_3 + D_1 D_2'$

 





Outline


- Decoder
- Multiplexer
- Encoder
- **Gate Behavior**

Gate Delays

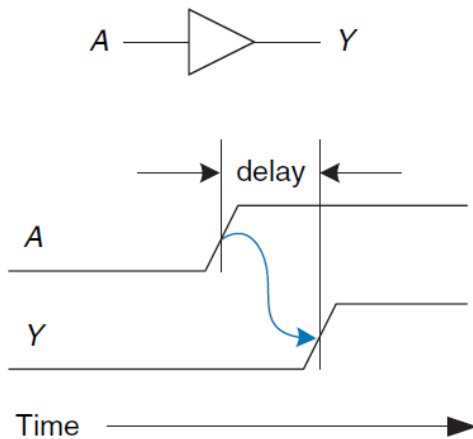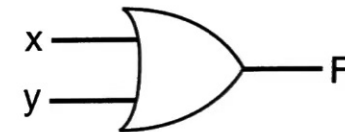- When the input to a logic gate is changed, the output will not change immediately. The output of the gate experiences a **propagation delay** in response to changes in the input.




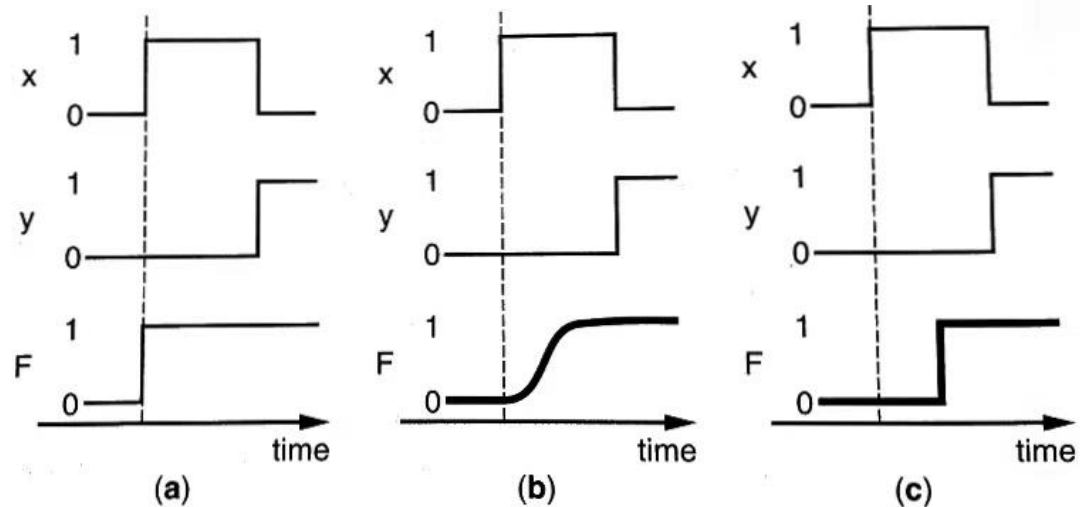
delay between an input change and the subsequent output change for a buffer



  - (a) ideal behavior without gate delay
(b) a more realistic illustration
(c) switching incorporating the delay

Effect of gate delays


- The analysis of a combinational circuit ignoring delays can predict only its **steady-state behavior**.
- Predicts a circuit's output as a function of its inputs assuming that the inputs have been stable for a long time, relative to the delays in the circuit's electronics.
- Because of circuit delays, the **transient behavior** of a combinational logic circuit may differ from what is predicted by steady-state analysis.




assume each gate has a propagation delay of 20 ns

Hazard (Glitches)

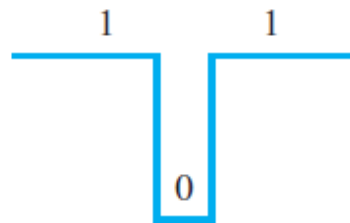- **Timing hazard**: **Unwanted** switching transients (glitches) appearing in the output while the input to a combinational circuit changes.
 - **static-1 hazard** is a short **0** glitch when for a changed input, we expect (by logic theorems) the output to remain constant **1**.
 - **static-0 hazard** is a short **1** glitch when we expect the output to remain constant **0**.




(a) Static 1-hazard

 

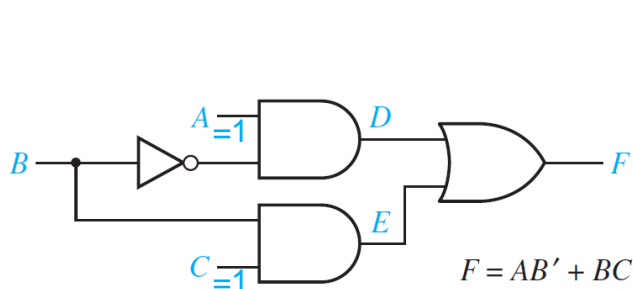(b) Static 0-hazard



Circuit with a static 1 Hazard

- Assume each gate has a propagation delay of 10 ns
 - if $A = C = 1$ and B changes from 1 to 0, F should be a stable 1. Change propagates to output F along two paths with different delays, resulting in a glitch in F .



| BC | | B | | | |
|----|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| A | 0 | 0 | 0 | 1 | 0 |
| | 1 | 1 | 1 | 1 | 0 |
| | | C | | | |


If any two adjacent 1's are not covered by the same circle, a 1-hazard exists for the transition between the two 1's.

 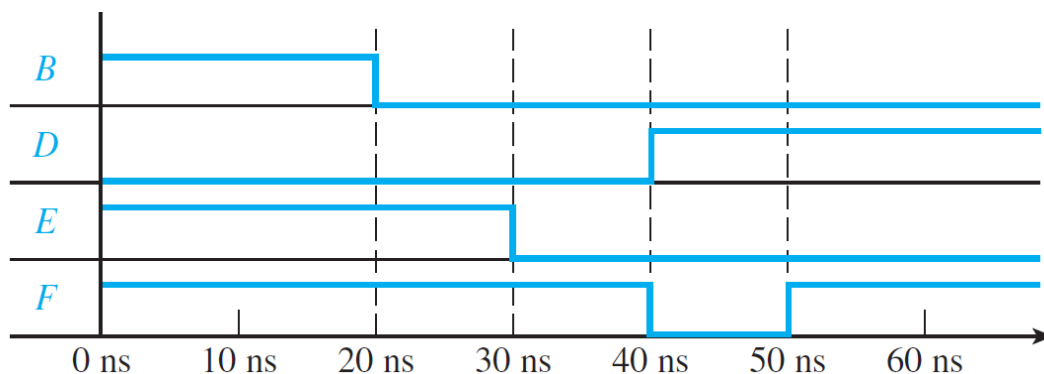


Static 1-hazard

Circuit with a static 0 Hazard


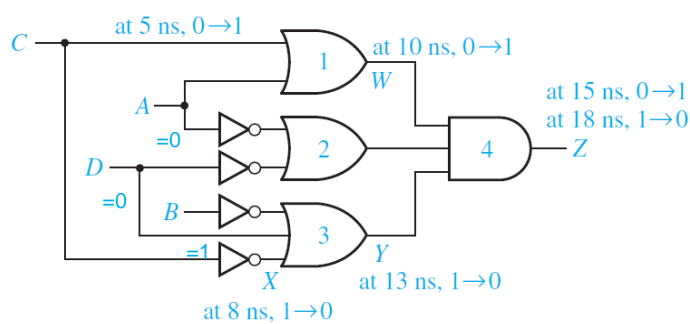
- Assume gate delay: Inverter = 3ns, AND/OR = 5ns
 - if $A = 0$, $B = 1$, $D = 0$, and C changes from 0 to 1, F should be a stable 0. Change propagates to output F along two paths with different delays., resulting in a glitch in F .



$$F = (A + C)(A' + D')(B' + C' + D)$$

 


If any two adjacent 0's are not covered by the same circle, a 0-hazard exists for the transition between the two 0's.

  


Static 0-hazard

Removing Hazard

 
- We can eliminate the 1-hazard or 0-hazards by adding additional circle that covers the adjacent 1's or 0's not already covered within a common circle.



Term AC is added to eliminate 1 hazard

 


$$F = AB' + BC + AC$$

 

Term $(C+D')$, $(A+B'+D)$, $(A'+B'+C')$ are added to eliminate 1 hazard


 
Example

- What happens when $A = 0$, $C = 1$, B falls?



| | | AB | | | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| C | 0 | 1 | 0 | 0 | 0 |
| | 1 | 1 | 1 | 1 | 0 |

$$Y = A'B' + BC$$

 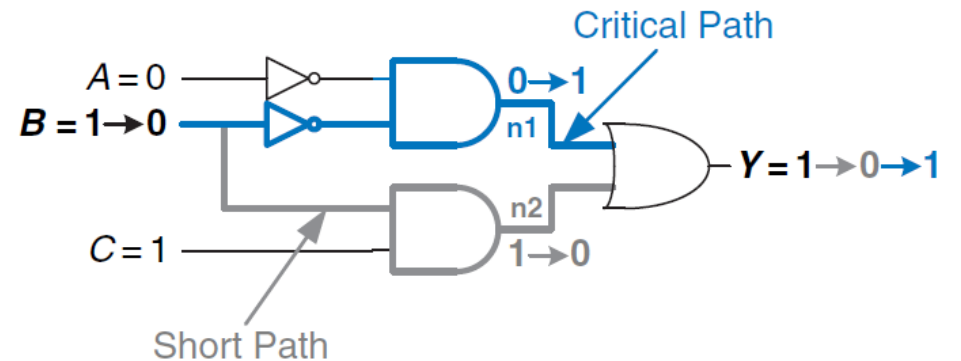

Example


- To eliminate the 1-hazard, add an additional circles that cover the adjacent 1's not already covered by a common circle.

| Y C | AB | | | |
|--------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

Minimal cost
but with hazard:
 $Y = A'B' + BC$

| Y C | AB | | | |
|--------|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |


$Y = A'B' + BC + A'C$

 

Eliminate hazard by
adding a product term


Testing of Logic Circuits

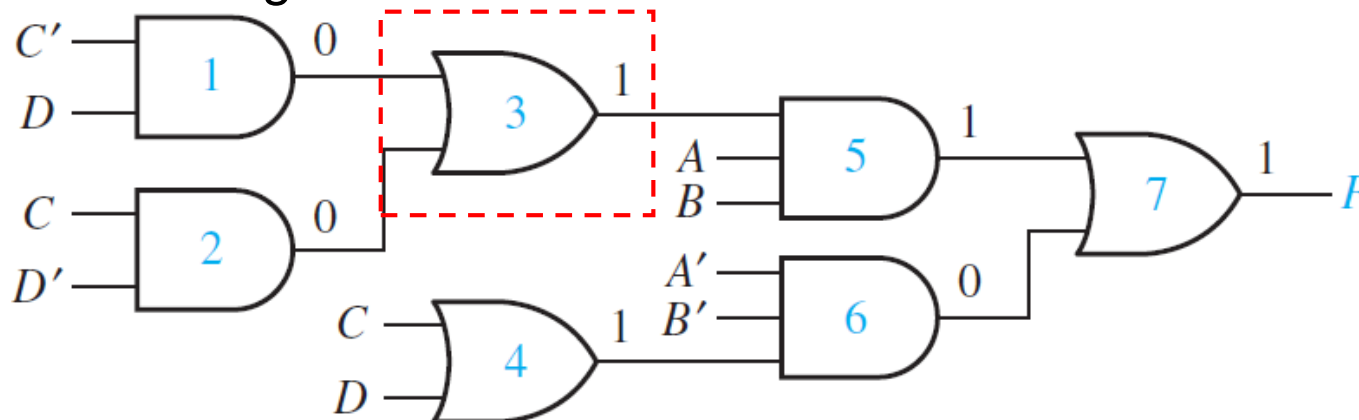- In the logic circuit, a wrong output may be due to
 - Incorrect design
 - Gates connected wrong
 - Wrong input signals to the circuit
 - Defective gates
 - Defective connecting wires
- Logic circuit with incorrect output
 - $A = B = C = D = 1$, F should be 0 but an incorrect 1 is generated, what's wrong?





Tri-state

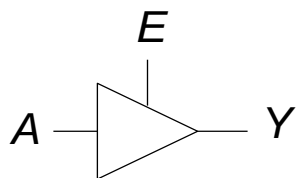- Tri-state driver (buffer) has three possible output states: 0, 1, Z (high impedance).



| E | A | Y |
|-----|-----|-----|
| 0 | 0 | Z |
| 0 | 1 | Z |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

 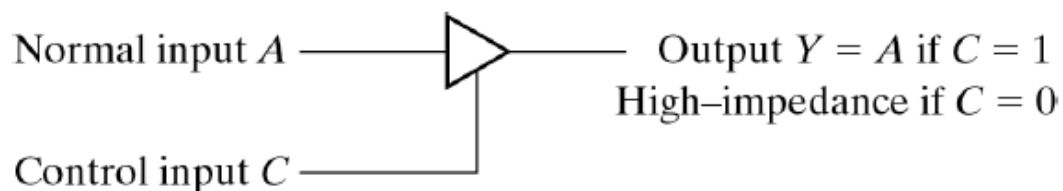

2:1 MUX using tri-state

| Sel | Y |
|-----|-----|
| 0 | A |
| 1 | B |